




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14137625
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS EMMANUEL MORALES MENUIOLA		

Answers

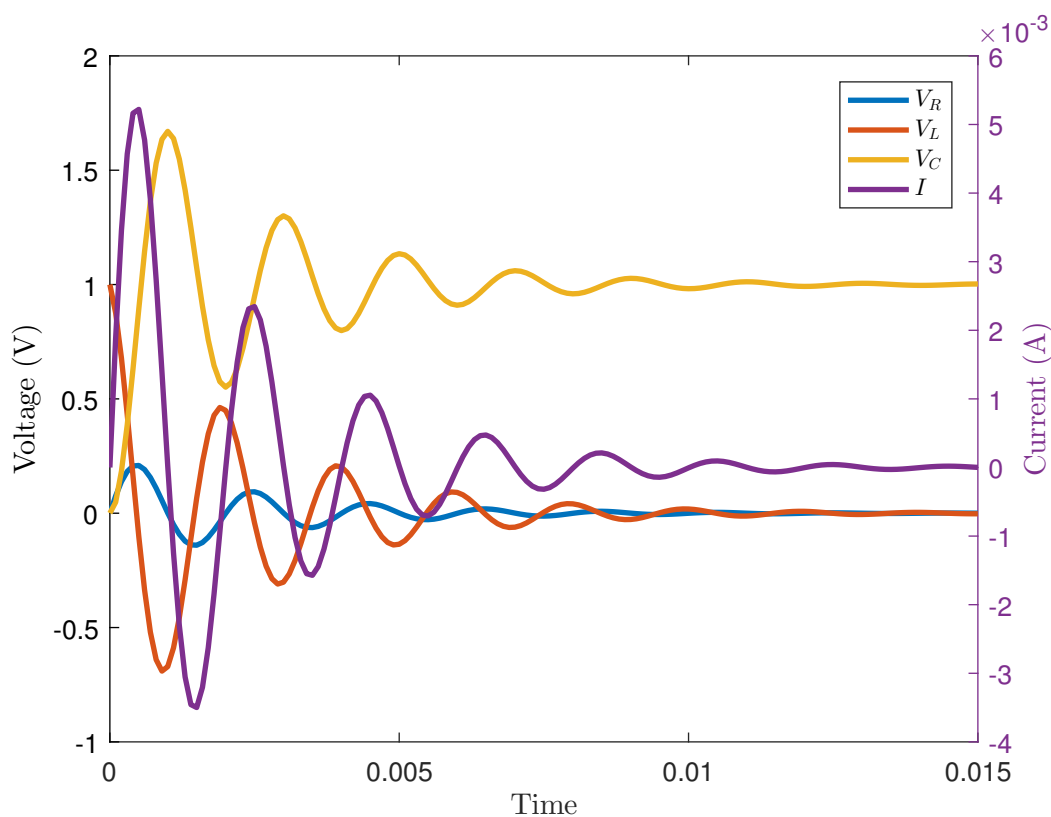1. The following figure shows the results.



2. The resonant frequency is $f_R = 503.2921$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14121732
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOEL GERARDO AGUERO LLANAS		

Answers

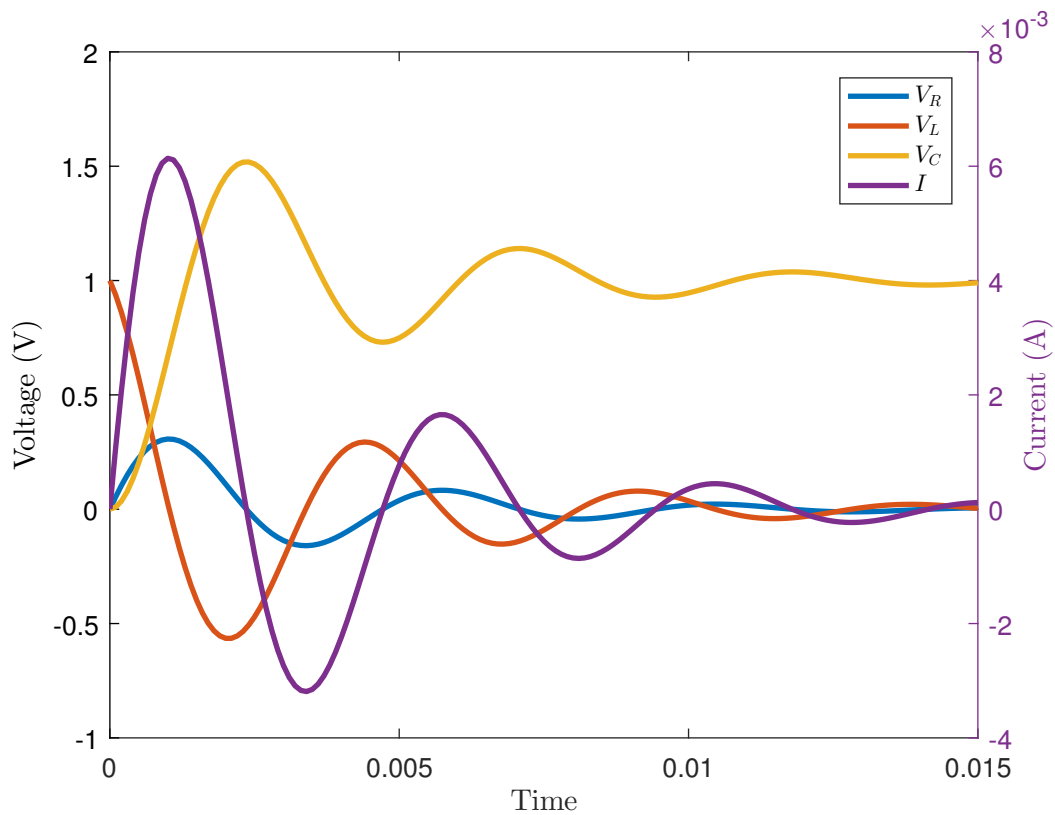1. The following figure shows the results.



2. The resonant frequency is $f_R = 216.5824$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14124427
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JERSON CHAVEZ ORTIZ		

Answers

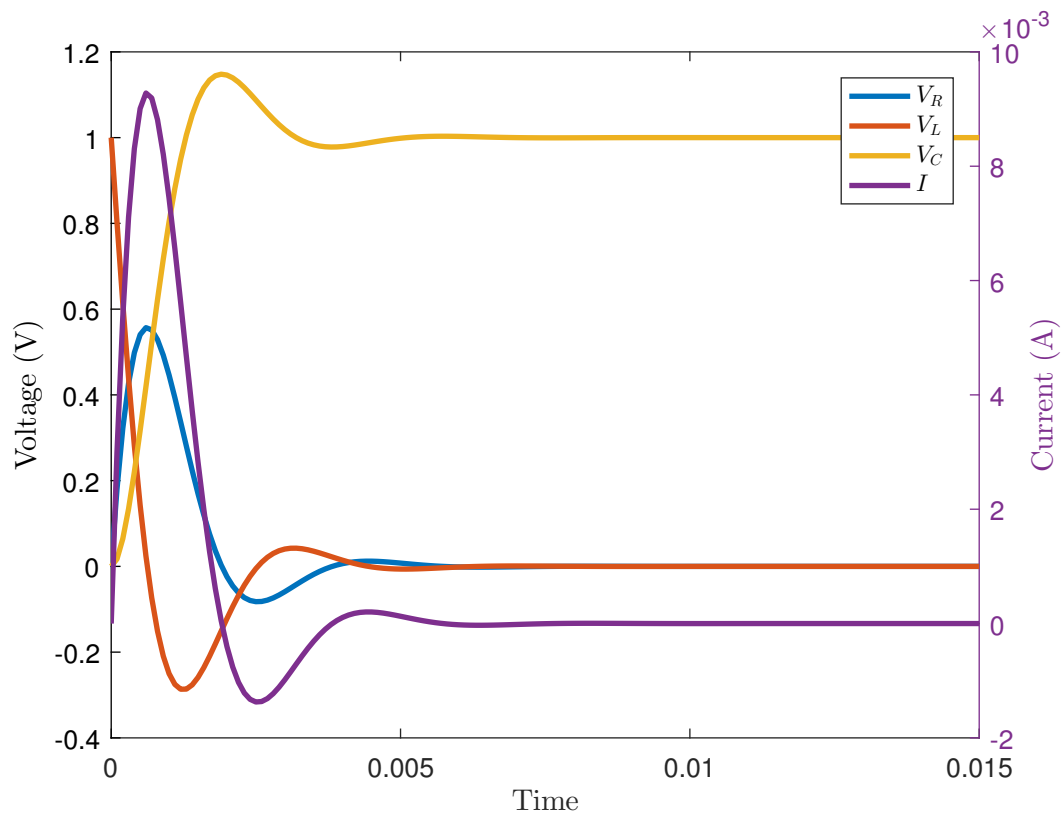1. The following figure shows the results.



2. The resonant frequency is $f_R = 306.2938$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14156040
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ANTONIO FERNENDEZ CARRASCO		

Answers

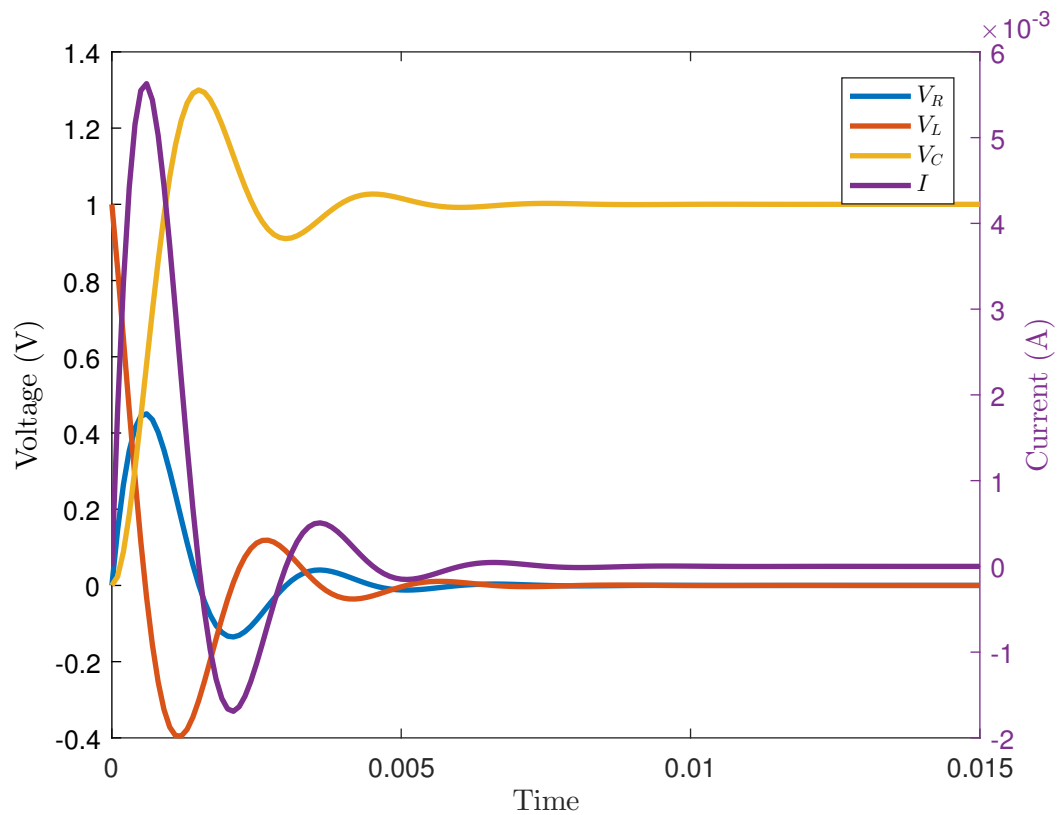1. The following figure shows the results.



2. The resonant frequency is $f_R = 355.8813$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14156037
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	MICHAEL MURILLO MENDEZ		

Answers

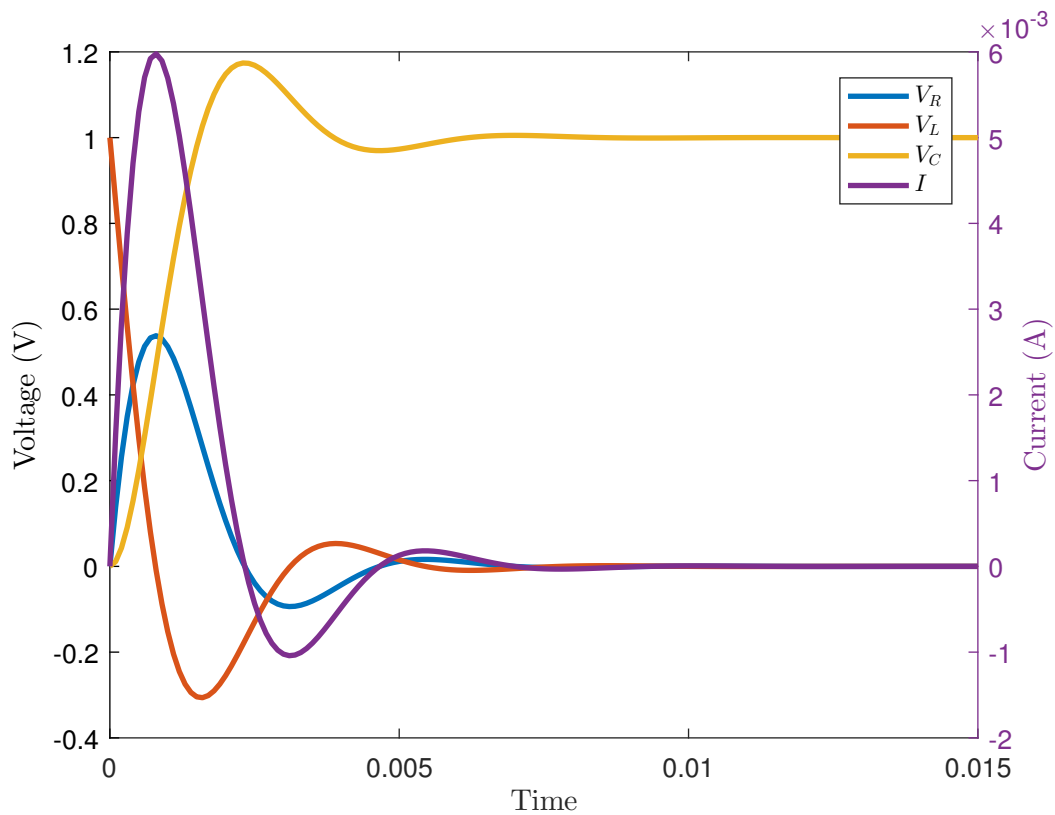1. The following figure shows the results.



2. The resonant frequency is $f_R = 245.5814$ Hz.



Universidad Autónoma de Coahuila


Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	11073892
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSUE AMADOR SIFUENTES		

Answers

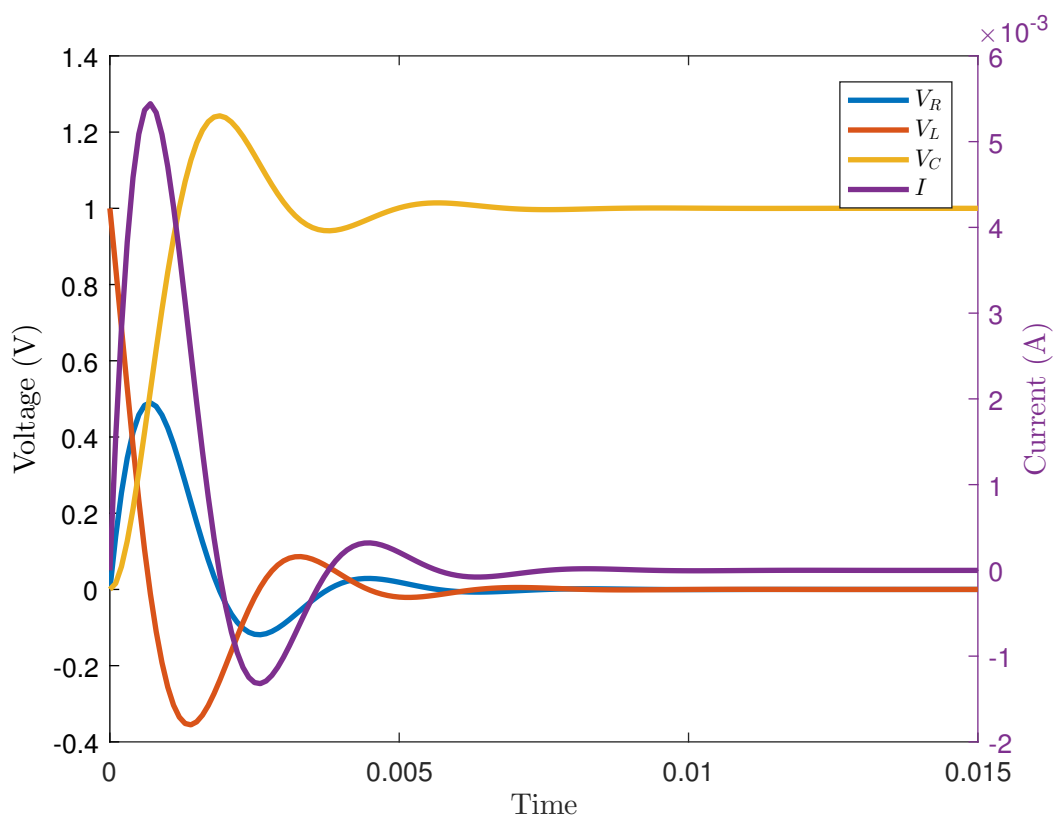- The following figure shows the results.



- The resonant frequency is $f_R = 290.5758$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	11268436
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDUARDO ZALDIVAR MARTINEZ		

Answers

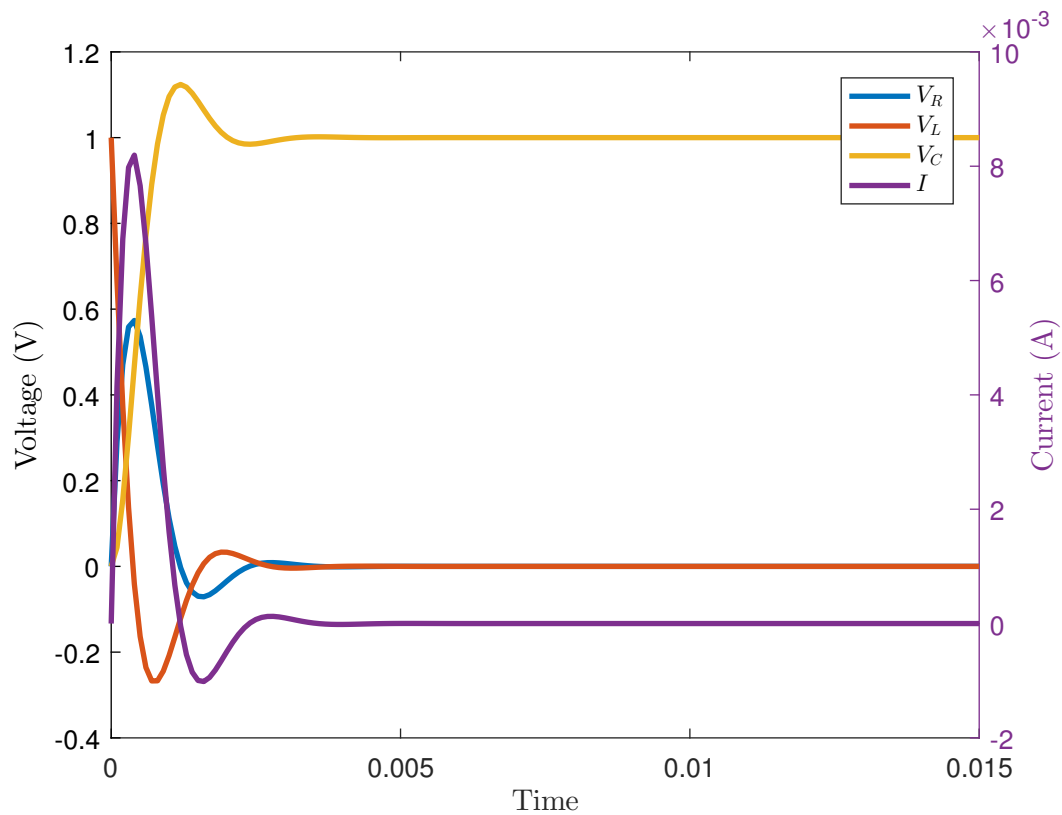1. The following figure shows the results.



2. The resonant frequency is $f_R = 503.2921$ Hz.



Universidad Autónoma de Coahuila


Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14140390
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS DAVID MARENTES REYES		

Answers

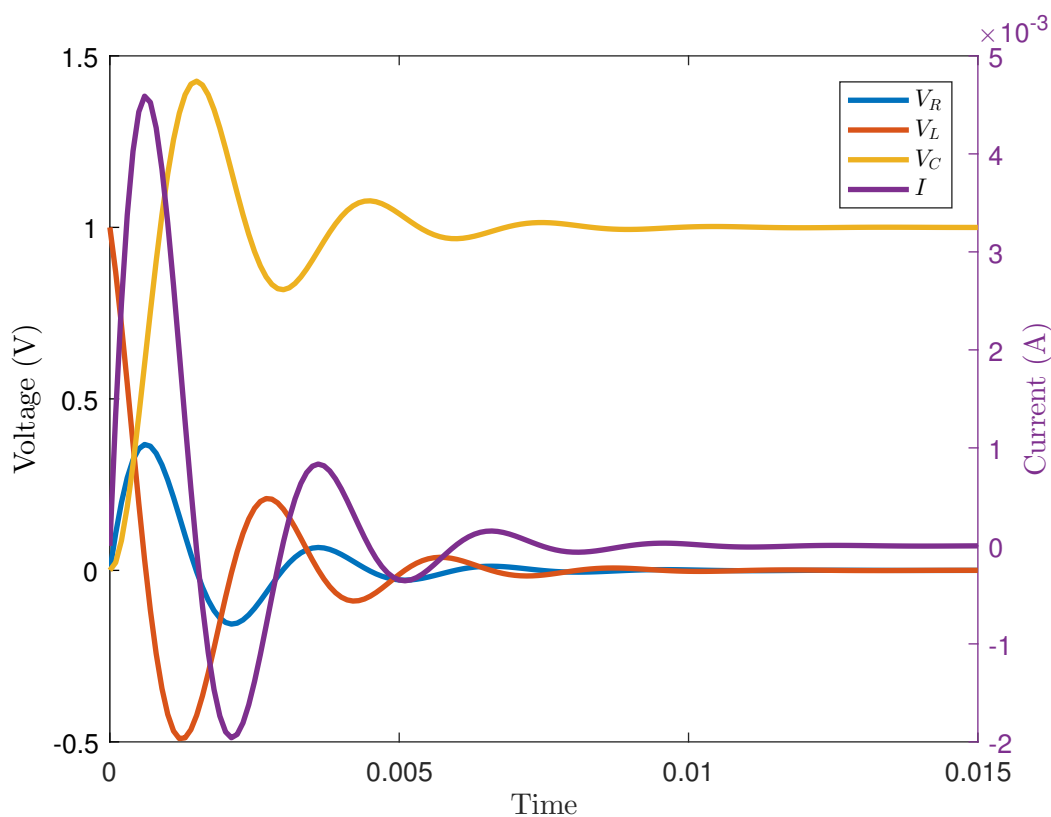- The following figure shows the results.



- The resonant frequency is $f_R = 347.3046$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	12068799
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS ANTONIO ROBLESREYES		

Answers

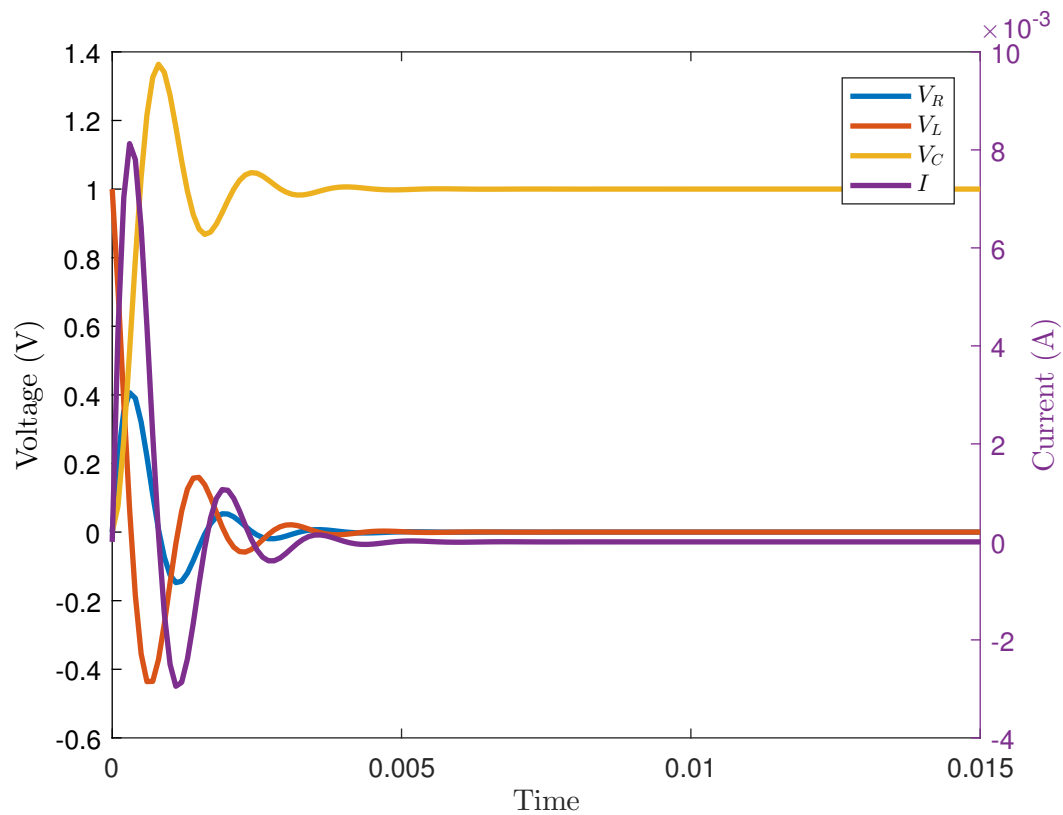1. The following figure shows the results.



2. The resonant frequency is $f_R = 649.7473$ Hz.



Universidad Autónoma de Coahuila


Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14150725
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LILIANA VERA GLZ		

Answers

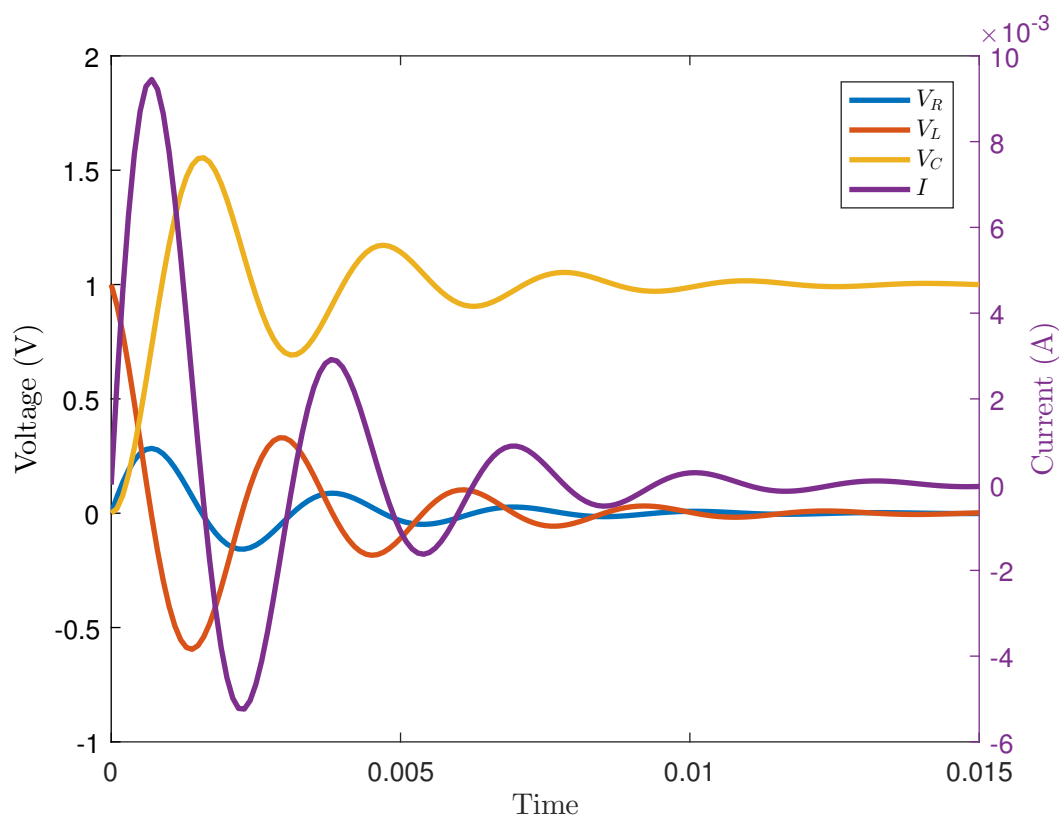- The following figure shows the results.



- The resonant frequency is $f_R = 324.8737$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14125016
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	DAVID OTHONIEL SALDIVAR PEREZ		

Answers

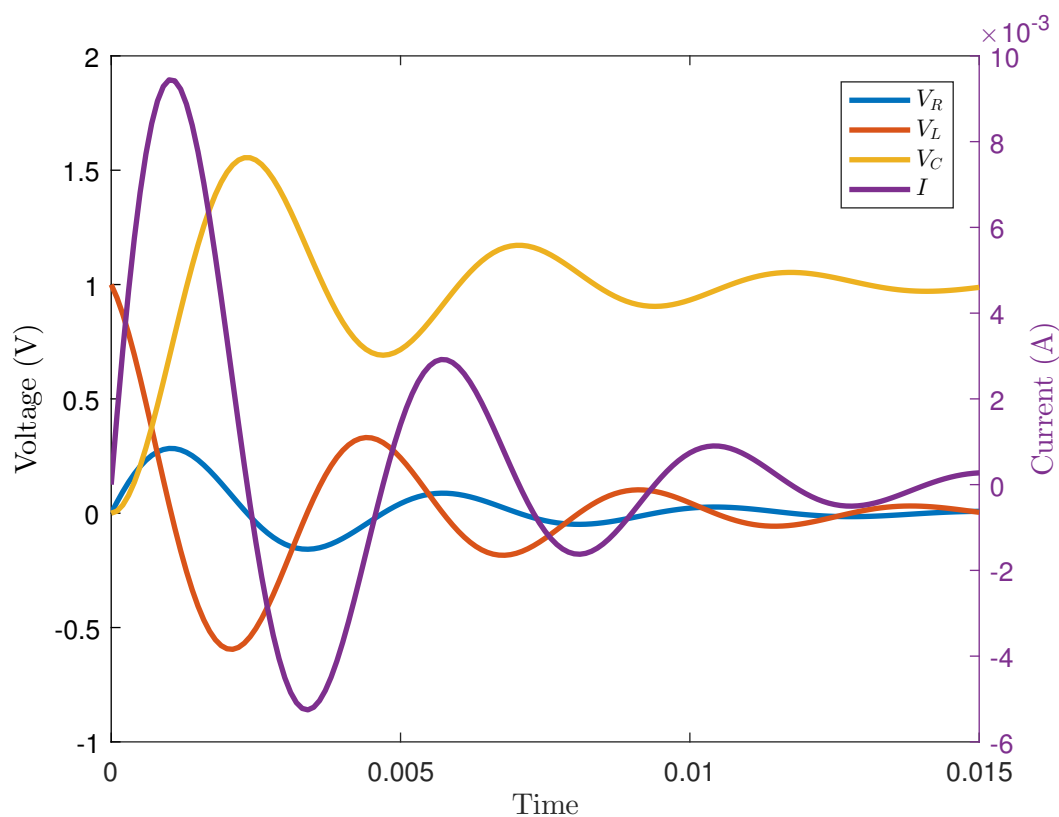1. The following figure shows the results.



2. The resonant frequency is $f_R = 216.5824$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	1205596
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ALBERTO VAZQUEZ MEDINA		

Answers

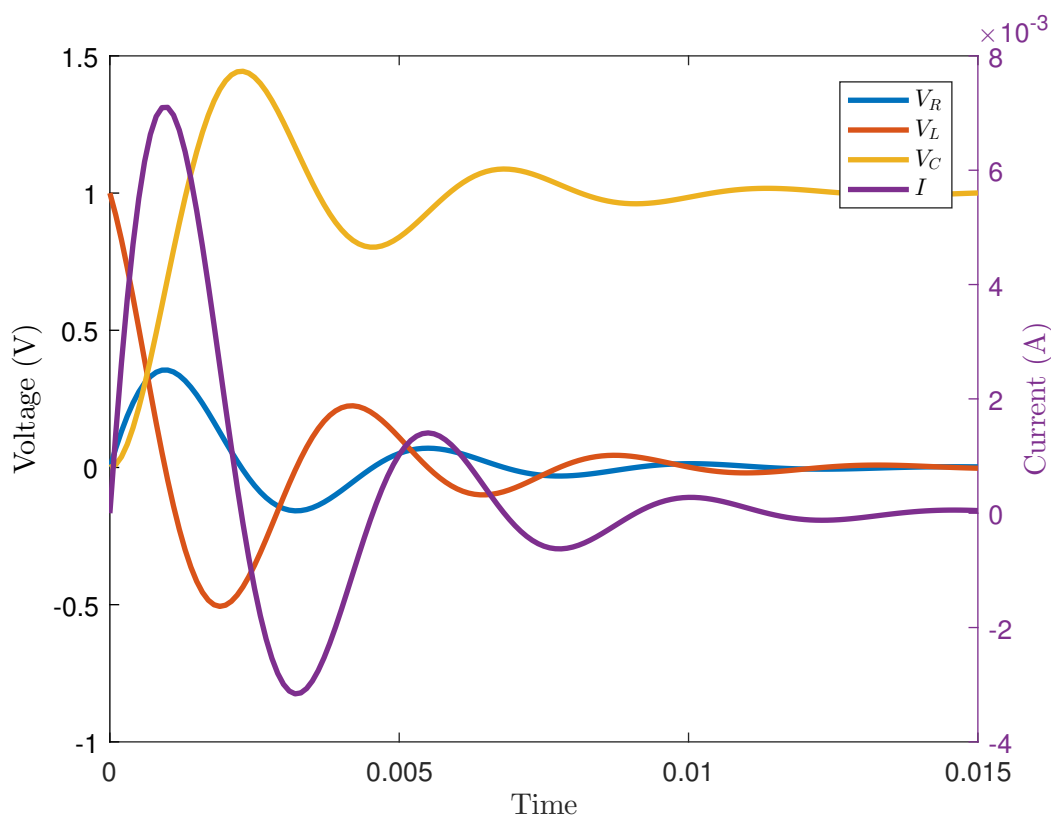1. The following figure shows the results.



2. The resonant frequency is $f_R = 227.3642$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	12666518
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	SAMUEL ROSAS GONZALEZ		

Answers

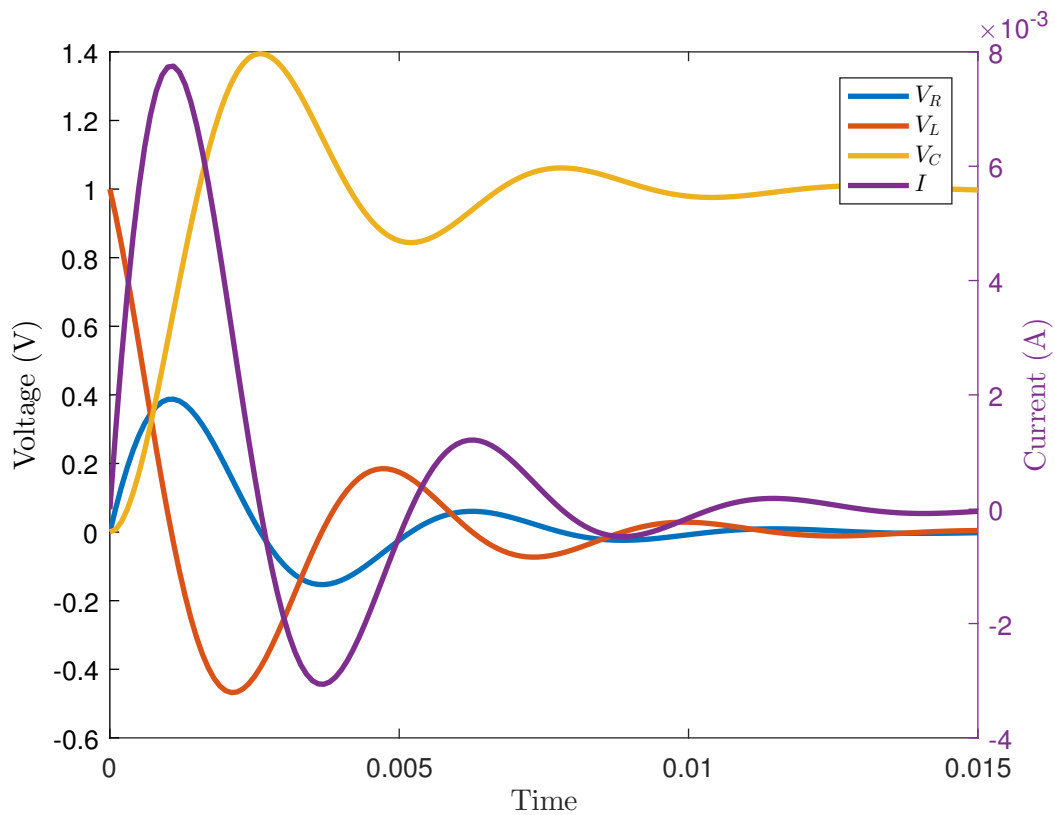1. The following figure shows the results.



2. The resonant frequency is $f_R = 200.5164$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	12064655
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDSON ORLANDONAVARRO RAMIREZ		

Answers

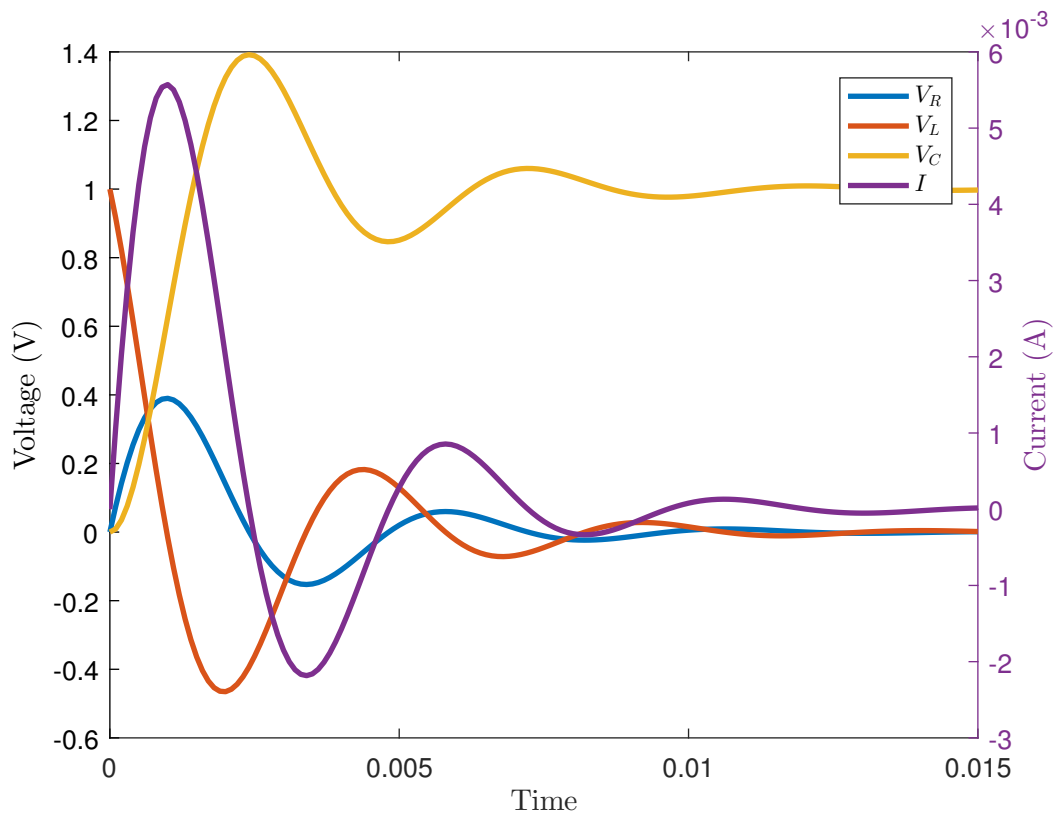1. The following figure shows the results.



2. The resonant frequency is $f_R = 216.5824$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	11126870
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN GAEL GONZALEZ RODRIGUEZ		

Answers

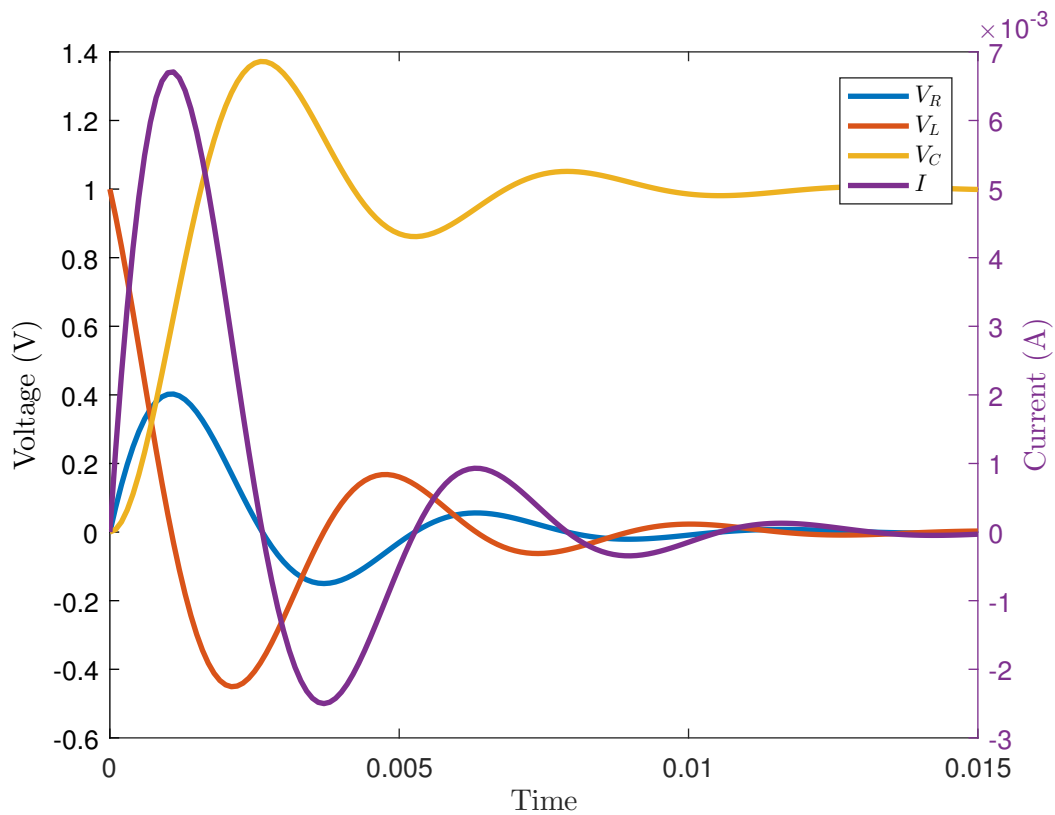1. The following figure shows the results.



2. The resonant frequency is $f_R = 198.9437$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14155580
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ALEJANDRO URBINA GONZALEZ		

Answers

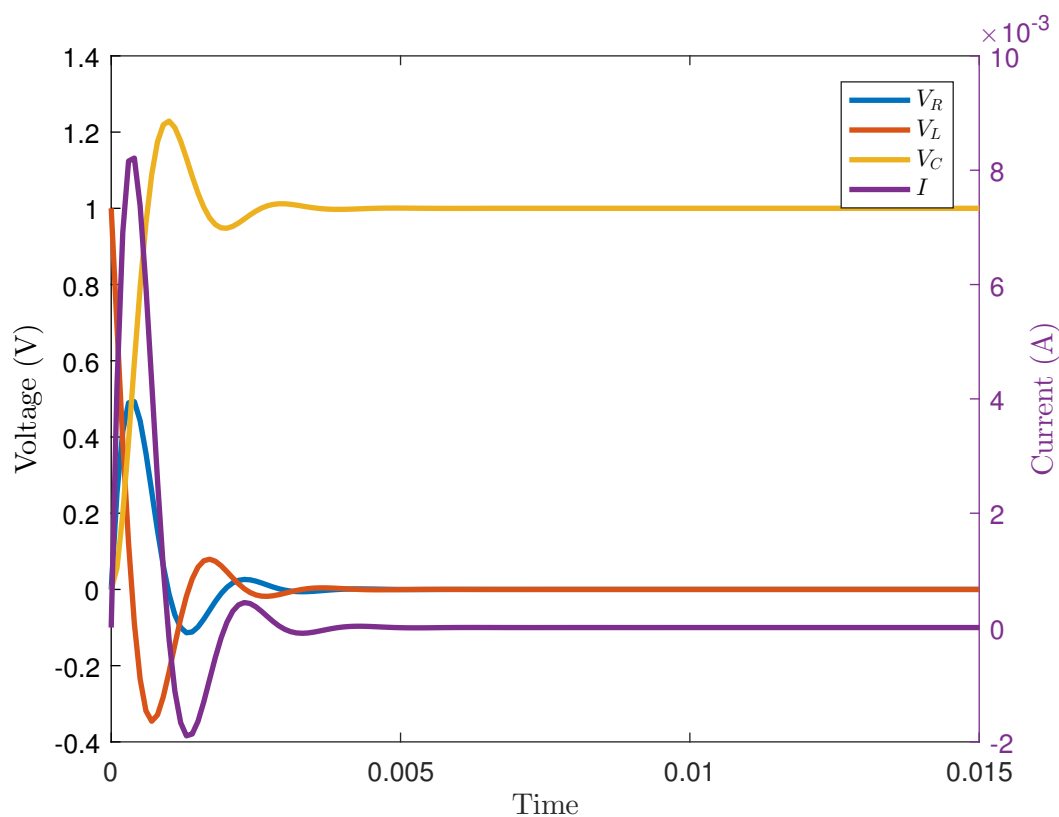1. The following figure shows the results.



2. The resonant frequency is $f_R = 562.6977$ Hz.




Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	11/11/2016
Exam / Homework	Exam 2 (Max time: One hour)	Registration #	14629184
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSE WALDO QUINTANA ARANDA		

Answers

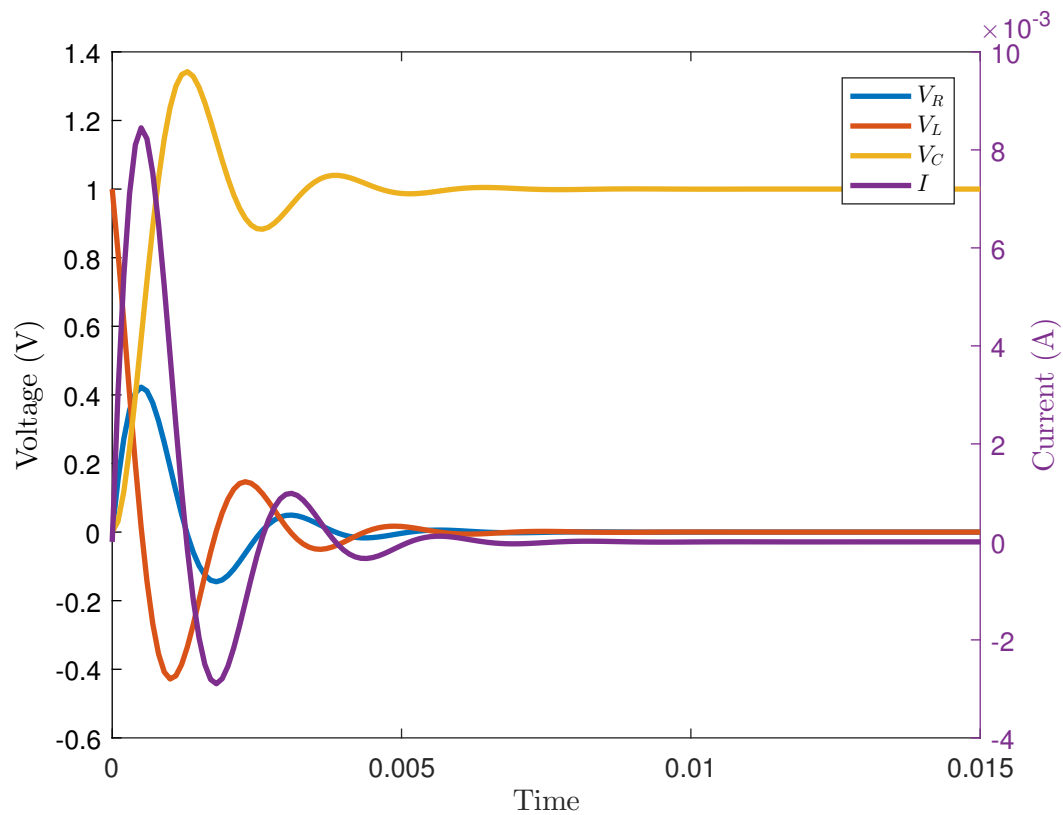1. The following figure shows the results.



2. The resonant frequency is $f_R = 410.9363$ Hz.