



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|--|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14137625 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | JESUS EMMANUEL MORALES MENUIOLA | | |

Answers

1. $R_{AB} = (9.333\ 33 + j13.3333)\ \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14121732 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | JOEL GERARDO AGUERO LLANAS | | |

Answers

1. $R_{AB} = (14 + j22.6667) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14124427 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | JERSON CHAVEZ ORTIZ | | |

Answers

1. $R_{AB} = (18 + j10.6667) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|--|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14156040 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | LUIS ANTONIO FERNENDEZ CARRASCO | | |

Answers

1. $R_{AB} = (18.6667 + j14) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14156037 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | MICHAEL MURILLO MENDEZ | | |

Answers

1. $R_{AB} = (22.6667 + j13.3333) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 11073892 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | JOSUE AMADOR SIFUENTES | | |

Answers

1. $R_{AB} = (21.3333 + j14.6667) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 11268436 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | EDUARDO ZALDIVAR MARTINEZ | | |

Answers

1. $R_{AB} = (17.3333 + j7.3333) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14140390 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | LUIS DAVID MARENTES REYES | | |

Answers

1. $R_{AB} = (18 + j18.6667) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 12068799 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | JESUS ANTONIO ROBLESREYES | | |

Answers

1. $R_{AB} = (12 + j8.666\ 67)\ \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14150725 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | LILIANA VERA GLZ | | |

Answers

1. $R_{AB} = (10 + j14) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|--------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14125016 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | DAVID OTHONIEL SALDIVAR PEREZ | | |

Answers

1. $R_{AB} = (12 + j15.3333) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 1205596 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | ALBERTO VAZQUEZ MEDINA | | |

Answers

1. $R_{AB} = (14.6667 + j19.3333) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 12666518 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | SAMUEL ROSAS GONZALEZ | | |

Answers

1. $R_{AB} = (16 + j17.3333) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 12064655 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | EDSON ORLANDONAVARRO RAMIREZ | | |

Answers

1. $R_{AB} = (18 + j24) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 11126870 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | JUAN GAEL GONZALEZ RODRIGUEZ | | |

Answers

1. $R_{AB} = (17.3333 + j22) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|---------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14155580 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | LUIS ALEJANDRO URBINA GONZALEZ | | |

Answers

1. $R_{AB} = (14.6667 + j6.6667) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

| | | | |
|------------------|-------------------------------------|----------------|-----------------|
| Subject | Circuit analysis II | Group | 5A |
| Degree | Electrical engineering | Due for | 4/10/2016 |
| Exam / Homework | Homework 3: Nodal and Mesh analysis | Registration # | 14629184 |
| Professor's name | Dr. Suresh Kumar Gadi | Marks Obtained | ____ / 10 |
| Student's name | JOSE WALDO QUINTANA ARANDA | | |

Answers

1. $R_{AB} = (13.3333 + j8.66667) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.