



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Industrial electronics	Group	9B
Degree	Mechanical engineering	Date	16/03/2017
Exam / Homework	Homework 4: Switched-mode power supply (SMPS)	Registration #	12717949
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN CARLOS BARRIENTOS GUERRA		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Simulate the following circuits. Present circuit diagram and output waveform.
 - (a) Buck converter (2.5 points)
 - (b) Boost converter (2.5 points)
 - (c) Buck-boost converter (2.5 points)
 - (d) Ćuk converter (2.5 points)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Industrial electronics	Group	9B
Degree	Mechanical engineering	Date	16/03/2017
Exam / Homework	Homework 4: Switched-mode power supply (SMPS)	Registration #	8062187
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	PÉREZ-FIGUEROA MAEDA CARLOS ARTURO		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Simulate the following circuits. Present circuit diagram and output waveform.
 - (a) Buck converter (2.5 points)
 - (b) Boost converter (2.5 points)
 - (c) Buck–boost converter (2.5 points)
 - (d) Ćuk converter (2.5 points)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Industrial electronics	Group	9B
Degree	Mechanical engineering	Date	16/03/2017
Exam / Homework	Homework 4: Switched-mode power supply (SMPS)	Registration #	12112592
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ROGELIO FLORES SALAZAR		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Simulate the following circuits. Present circuit diagram and output waveform.
 - (a) Buck converter (2.5 points)
 - (b) Boost converter (2.5 points)
 - (c) Buck-boost converter (2.5 points)
 - (d) Ćuk converter (2.5 points)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Industrial electronics	Group	9B
Degree	Mechanical engineering	Date	16/03/2017
Exam / Homework	Homework 4: Switched-mode power supply (SMPS)	Registration #	12122623
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	RAÚL ALEXANDRO ARELLANO SALCIDO		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Simulate the following circuits. Present circuit diagram and output waveform.
 - (a) Buck converter (2.5 points)
 - (b) Boost converter (2.5 points)
 - (c) Buck–boost converter (2.5 points)
 - (d) Ćuk converter (2.5 points)