



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	9132341
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDGAR CERDA PEREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 7 + 4j$, $B = 5 + 7j$ and $C = 8 + 7j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 4}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 2 m. The resistance of the metal frame used for the cube is $3 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

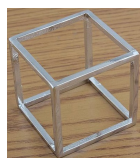


Figure 1


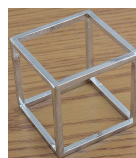


Figure 2

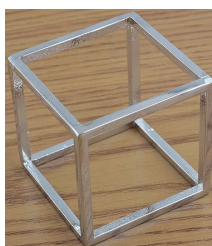3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	8053323
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN PABLO DUARTE MONSIVAIS		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 2 + 8j$, $B = 3 + 6j$ and $C = 5 + 4j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 8}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 5 m. The resistance of the metal frame used for the cube is $2 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

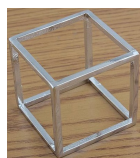


Figure 1


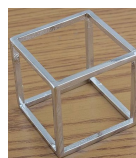


Figure 2

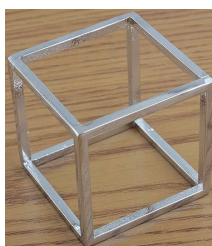3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12127844
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN MIGUEL BARRIENTOS GARCIA		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 5 + 2j$, $B = 7 + 8j$ and $C = 5 + 7j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 2}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 9 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

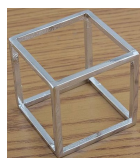


Figure 1


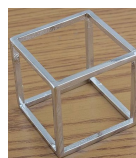


Figure 2

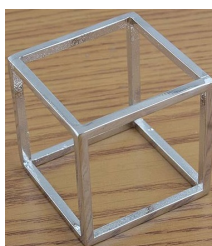3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12132791
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ISRAEL GONZALEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 3 + 3j$, $B = 7 + 6j$ and $C = 5 + 5j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 3}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 7 m. The resistance of the metal frame used for the cube is $7 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

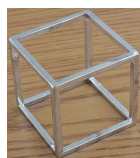


Figure 1


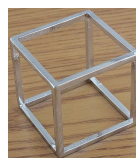


Figure 2

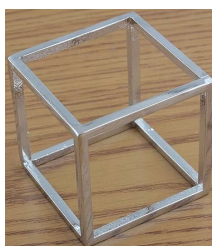3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	10062268
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<i>JULIO ALEJANDRO MARIN GARCIA</i>		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 6 + 4j$, $B = 7 + 9j$ and $C = 8 + 4j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 4}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 4 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

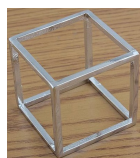


Figure 1


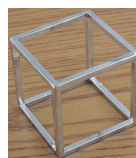


Figure 2

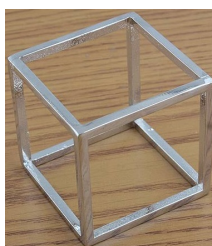3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	7050612
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	BEATRIZ ELIZABETH ALBA PEREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 6 + 4j$, $B = 9 + 3j$ and $C = 8 + 2j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 4}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 8 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

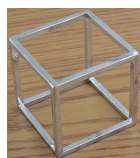


Figure 1


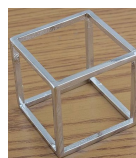


Figure 2

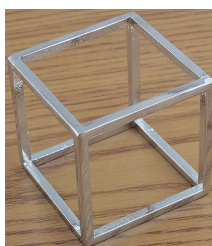3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	98017052
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIZ EDUARDO		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 6 + 3j$, $B = 4 + 7j$ and $C = 8 + 5j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 3}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 2 m. The resistance of the metal frame used for the cube is $5 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

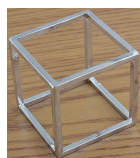


Figure 1


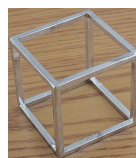


Figure 2

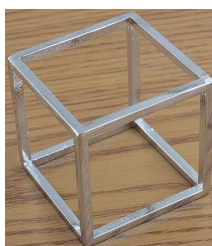3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12125213
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EMMANUEL ALEJANDRO		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 8 + 3j$, $B = 9 + 3j$ and $C = 4 + 3j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 3}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 4 m. The resistance of the metal frame used for the cube is $7 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

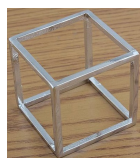


Figure 1


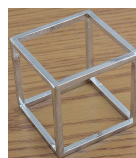


Figure 2

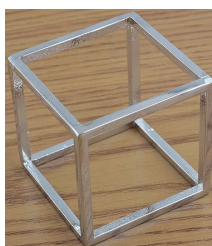3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12146394
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSELY ROSALES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 5 + 4j$, $B = 3 + 2j$ and $C = 8 + 3j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 4}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 8 m. The resistance of the metal frame used for the cube is $5 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

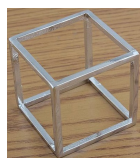


Figure 1


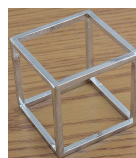


Figure 2

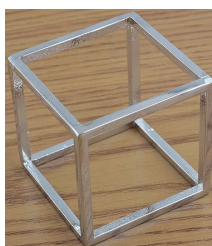3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12133449
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	MARIO ALBERTO GAMEZ ROQUE		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 3 + 2j$, $B = 4 + 8j$ and $C = 7 + 4j$, simplify the following expressions. (2 points)
 - (a) A^3
 - (b) $\frac{A^2 B}{C}$
 - (c) $\frac{A}{B} + C$
 - (d) $\frac{A}{\frac{B}{C} + 2}$
2. The side of the cube-shaped metal frame shown in Figure 1 is 4 m. The resistance of the metal frame used for the cube is $2 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

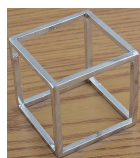


Figure 1


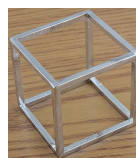


Figure 2

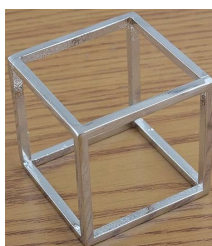3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12146385
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	RODRIGUEZ PEREZ RODOLFO		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 8 + 8j$, $B = 5 + 3j$ and $C = 8 + 6j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 8}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 6 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

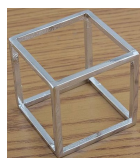


Figure 1


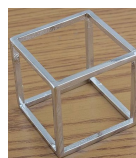


Figure 2

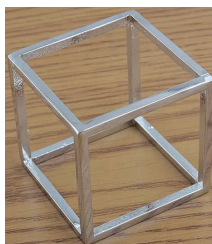3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	10056986
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ARTURO CORDERO ROBLES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 4 + 9j$, $B = 6 + 7j$ and $C = 2 + 3j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 9}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 9 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

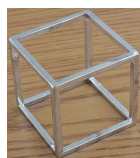


Figure 1


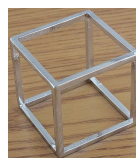


Figure 2

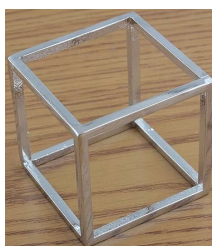3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12128743
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	GIBRAM ALFONSO HERNANDEZ MARTINEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 9 + 7j$, $B = 8 + 6j$ and $C = 8 + 6j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 7}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 9 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

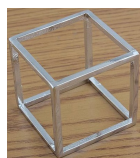


Figure 1


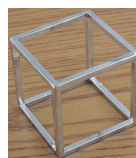


Figure 2

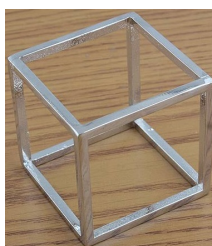3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12157333
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDGAR RICARDO CHAIREZ VILLARRIAL		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 3 + 4j$, $B = 7 + 8j$ and $C = 4 + 3j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 4}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 9 m. The resistance of the metal frame used for the cube is $5 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

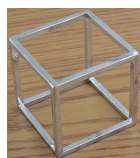


Figure 1


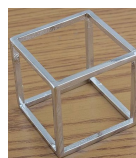


Figure 2

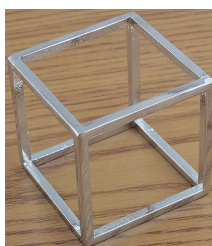3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12154267
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSE FRANCISCO TOVAR JARAMILLO-		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 2 + 9j$, $B = 4 + 9j$ and $C = 2 + 2j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 9}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 4 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

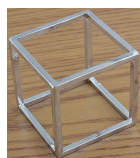


Figure 1


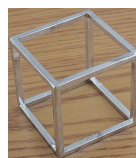


Figure 2

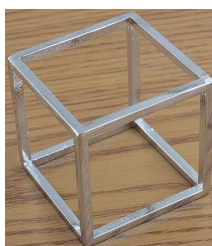3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12142724
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ALLISON DANIELA MACIAS HERNANDEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 8 + 6j$, $B = 7 + 4j$ and $C = 8 + 8j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 6}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 5 m. The resistance of the metal frame used for the cube is $2 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

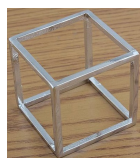


Figure 1


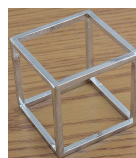


Figure 2

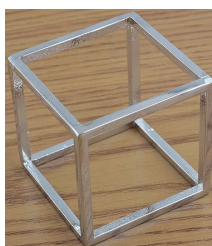3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	10068360
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	KIM EDUARDO SANCHEZ REYES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 9 + 2j$, $B = 8 + 8j$ and $C = 8 + 4j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 2}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 2 m. The resistance of the metal frame used for the cube is $5 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

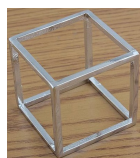


Figure 1


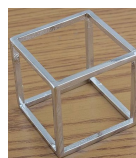


Figure 2

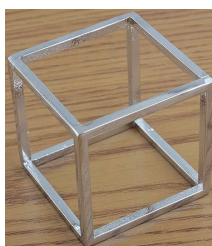3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	11288180
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JORGE ANTONIO MOLINA RAMIREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 6 + 9j$, $B = 6 + 8j$ and $C = 6 + 2j$, simplify the following expressions. (2 points)
 - (a) A^3
 - (b) $\frac{A^2 B}{C}$
 - (c) $\frac{A}{B} + C$
 - (d) $\frac{A}{\frac{B}{C} + 9}$
2. The side of the cube-shaped metal frame shown in Figure 1 is 8 m. The resistance of the metal frame used for the cube is $2 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

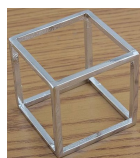


Figure 1


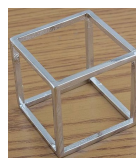


Figure 2

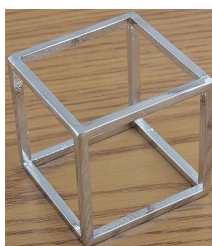3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12139200
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	CARLOS RODOLFO MENA MONTES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 5 + 6j$, $B = 5 + 2j$ and $C = 9 + 7j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 6}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 2 m. The resistance of the metal frame used for the cube is $5 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

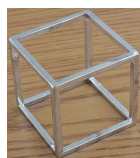


Figure 1


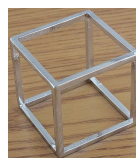


Figure 2

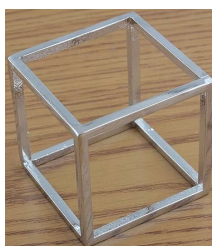3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	10053330
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSE FERNANDO AGUILAR COLORADO		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 4 + 6j$, $B = 5 + 7j$ and $C = 3 + 9j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 6}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 7 m. The resistance of the metal frame used for the cube is $8 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

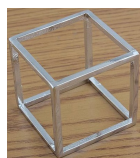


Figure 1


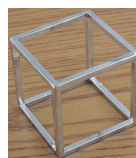


Figure 2

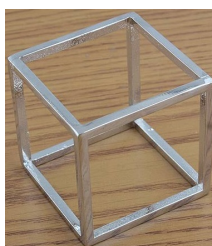3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	5113606
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	OBDULIA CASTANEDA PEREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 7 + 6j$, $B = 7 + 7j$ and $C = 6 + 3j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 6}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 2 m. The resistance of the metal frame used for the cube is $3 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

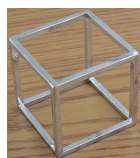


Figure 1


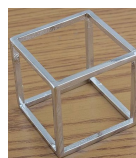


Figure 2

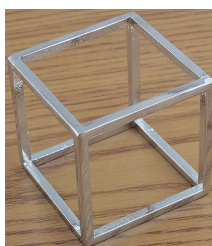3. Find the equivalent resistance of the circuit shown in Figure 2.





Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	10073388
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	AXEL JAVIER RODRIGUEZ MARIN		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Let $A = 2 + 3j$, $B = 9 + 4j$ and $C = 3 + 7j$, simplify the following expressions. (2 points)

(a) A^3 (b) $\frac{A^2 B}{C}$ (c) $\frac{A}{B} + C$ (d) $\frac{A}{\frac{B}{C} + 3}$

2. The side of the cube-shaped metal frame shown in Figure 1 is 2 m. The resistance of the metal frame used for the cube is $6 \Omega \text{ m}^{-1}$. Calculate the resistance between two opposite corners. (2 points)

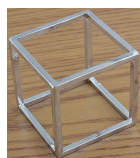


Figure 1

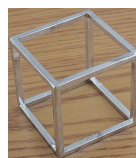


Figure 2

3. Find the equivalent resistance of the circuit shown in Figure 2.

