



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14137625</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>JESUS EMMANUEL MORALES MENUOLA</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.05$  s. The values are  $R = R_1 = R_2 = 40 \Omega$ ,  $L = 50$  mH,  $C = 200$   $\mu$ F and  $V_{AC} = 50$  V at 90 Hz. (3 + 3 points)

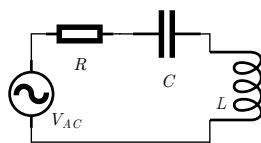

**Figure 1**

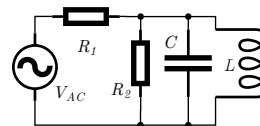

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 7 V and frequency 50 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 7 V and frequency 70 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 3 V and frequency 40 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 3 V and frequency 50 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 2 V and frequency 90 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 9 V and frequency 50 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 4 V, duty cycle 50 % and frequency 80 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14121732</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>JOEL GERARDO AGUERO LLANAS</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.02$  s. The values are  $R = R_1 = R_2 = 50 \Omega$ ,  $L = 90$  mH,  $C = 600$   $\mu$ F and  $V_{AC} = 70$  V at 20 Hz. (3 + 3 points)

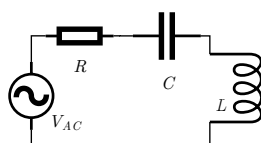

**Figure 1**

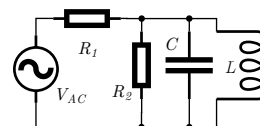

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 9 V and frequency 80 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 2 V and frequency 40 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 70 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 5 V and frequency 60 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 8 V and frequency 50 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 5 V and frequency 70 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 6 V, duty cycle 20 % and frequency 70 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14124427
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>JERSON CHAVEZ ORTIZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.05$  s. The values are  $R = R_1 = R_2 = 60 \Omega$ ,  $L = 30$  mH,  $C = 900$   $\mu$ F and  $V_{AC} = 70$  V at 30 Hz. (3 + 3 points)

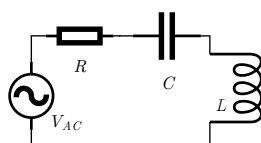

**Figure 1**

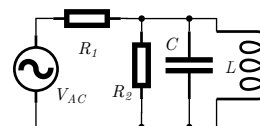

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 6 V and frequency 40 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 4 V and frequency 90 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 7 V and frequency 20 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 8 V and frequency 80 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 8 V and frequency 80 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 5 V and frequency 70 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 3 V, duty cycle 40 % and frequency 80 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14156040</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>LUIS ANTONIO FERNENDEZ CARRASCO</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.07$  s. The values are  $R = R_1 = R_2 = 80 \Omega$ ,  $L = 50$  mH,  $C = 400$   $\mu$ F and  $V_{AC} = 60$  V at 90 Hz. (3 + 3 points)

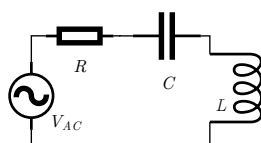

**Figure 1**

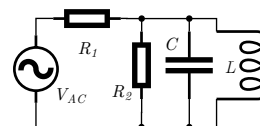

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 3 V and frequency 70 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 8 V and frequency 50 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 8 V and frequency 60 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 2 V and frequency 50 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 4 V and frequency 30 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 6 V, duty cycle 70 % and frequency 20 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14156037</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>MICHAEL MURILLO MENDEZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.06$  s. The values are  $R = R_1 = R_2 = 90 \Omega$ ,  $L = 60$  mH,  $C = 700$   $\mu$ F and  $V_{AC} = 20$  V at 70 Hz. (3 + 3 points)

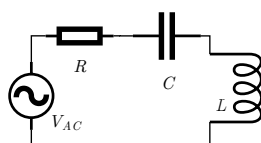

**Figure 1**

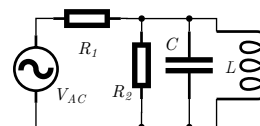

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 8 V and frequency 90 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 3 V and frequency 20 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 3 V and frequency 90 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 5 V and frequency 30 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 4 V and frequency 90 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 2 V and frequency 40 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 6 V, duty cycle 90 % and frequency 50 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>11073892</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>JOSUE AMADOR SIFUENTES</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.02$  s. The values are  $R = R_1 = R_2 = 90 \Omega$ ,  $L = 60$  mH,  $C = 500$   $\mu$ F and  $V_{AC} = 40$  V at 90 Hz. (3 + 3 points)

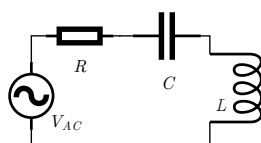

**Figure 1**

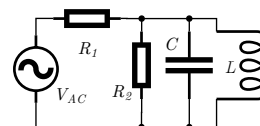

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 5 V and frequency 50 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 7 V and frequency 90 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 6 V and frequency 30 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 7 V and frequency 80 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 5 V and frequency 60 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 9 V and frequency 40 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 8 V, duty cycle 40 % and frequency 70 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>11268436</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>EDUARDO ZALDIVAR MARTINEZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.04$  s. The values are  $R = R_1 = R_2 = 70 \Omega$ ,  $L = 20$  mH,  $C = 500$   $\mu$ F and  $V_{AC} = 50$  V at 40 Hz. (3 + 3 points)

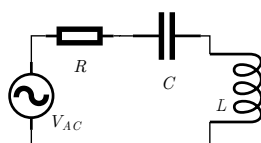

**Figure 1**

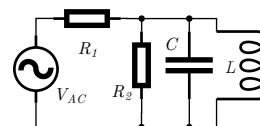

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 8 V and frequency 80 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 5 V and frequency 60 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 30 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 8 V and frequency 20 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 7 V and frequency 90 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 2 V and frequency 70 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 7 V, duty cycle 90 % and frequency 20 Hz. (0.5 point)





# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14140390</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>LUIS DAVID MARENTES REYES</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.03$  s. The values are  $R = R_1 = R_2 = 80 \Omega$ ,  $L = 70$  mH,  $C = 300$   $\mu$ F and  $V_{AC} = 70$  V at 80 Hz. (3 + 3 points)

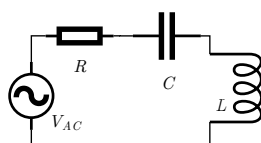

**Figure 1**

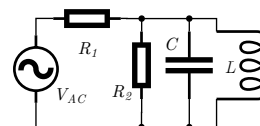

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 3 V and frequency 60 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 30 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 3 V and frequency 80 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 4 V and frequency 30 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 2 V and frequency 90 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 8 V and frequency 70 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 2 V, duty cycle 80 % and frequency 30 Hz. (0.5 point)





# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>12068799</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>JESUS ANTONIO ROBLESREYES</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.05$  s. The values are  $R = R_1 = R_2 = 50 \Omega$ ,  $L = 20$  mH,  $C = 300$   $\mu$ F and  $V_{AC} = 70$  V at 40 Hz. (3 + 3 points)

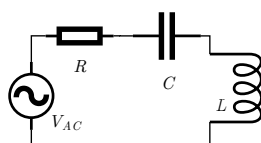

**Figure 1**

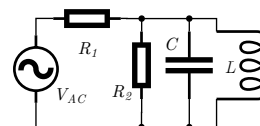

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 6 V and frequency 20 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 30 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 9 V and frequency 20 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 6 V and frequency 70 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 7 V and frequency 40 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 2 V and frequency 70 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 8 V, duty cycle 60 % and frequency 30 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14150725</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>LILIANA VERA GLZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.05$  s. The values are  $R = R_1 = R_2 = 30 \Omega$ ,  $L = 40$  mH,  $C = 600$   $\mu$ F and  $V_{AC} = 90$  V at 40 Hz. (3 + 3 points)

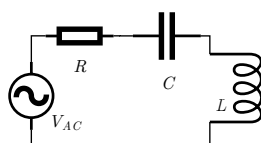

**Figure 1**

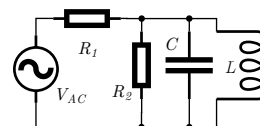

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 5 V and frequency 30 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 4 V and frequency 90 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 60 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 9 V and frequency 30 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 9 V and frequency 90 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 4 V and frequency 70 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 7 V, duty cycle 60 % and frequency 20 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14125016</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>DAVID OTHONIEL SALDIVAR PEREZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.02$  s. The values are  $R = R_1 = R_2 = 30 \Omega$ ,  $L = 60$  mH,  $C = 900$   $\mu$ F and  $V_{AC} = 50$  V at 40 Hz. (3 + 3 points)

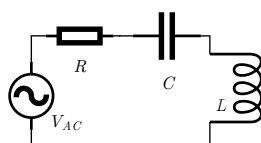

**Figure 1**

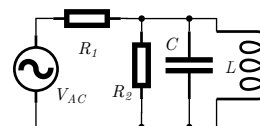

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 5 V and frequency 60 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 3 V and frequency 40 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 2 V and frequency 70 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 7 V and frequency 40 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 2 V and frequency 20 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 7 V and frequency 60 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 6 V, duty cycle 30 % and frequency 70 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>1205596</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>ALBERTO VAZQUEZ MEDINA</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.08$  s. The values are  $R = R_1 = R_2 = 50 \Omega$ ,  $L = 70$  mH,  $C = 700$   $\mu$ F and  $V_{AC} = 80$  V at 60 Hz. (3 + 3 points)

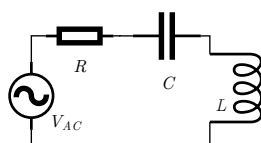

**Figure 1**

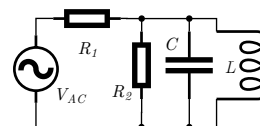

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 8 V and frequency 80 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 4 V and frequency 70 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 6 V and frequency 70 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 7 V and frequency 90 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 7 V and frequency 40 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 6 V, duty cycle 20 % and frequency 60 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>12666518</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>SAMUEL ROSAS GONZALEZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.03$  s. The values are  $R = R_1 = R_2 = 50 \Omega$ ,  $L = 70$  mH,  $C = 900$   $\mu$ F and  $V_{AC} = 50$  V at 70 Hz. (3 + 3 points)

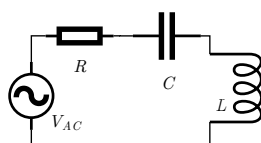

**Figure 1**

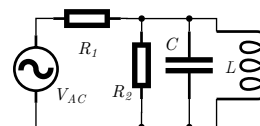

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 4 V and frequency 20 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 2 V and frequency 60 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 9 V and frequency 70 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 8 V and frequency 40 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 6 V and frequency 80 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 4 V, duty cycle 70 % and frequency 70 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>12064655</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>EDSON ORLANDONAVARRO RAMIREZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.07$  s. The values are  $R = R_1 = R_2 = 70 \Omega$ ,  $L = 90$  mH,  $C = 600$   $\mu$ F and  $V_{AC} = 90$  V at 40 Hz. (3 + 3 points)

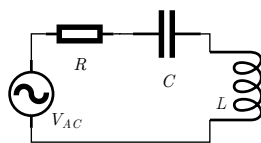

**Figure 1**

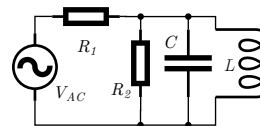

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 4 V and frequency 80 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 5 V and frequency 40 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 5 V and frequency 40 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 3 V and frequency 30 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 7 V and frequency 80 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 3 V and frequency 70 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 9 V, duty cycle 30 % and frequency 50 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>11126870</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>JUAN GAEL GONZALEZ RODRIGUEZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.06$  s. The values are  $R = R_1 = R_2 = 60 \Omega$ ,  $L = 80$  mH,  $C = 800$   $\mu$ F and  $V_{AC} = 90$  V at 90 Hz. (3 + 3 points)

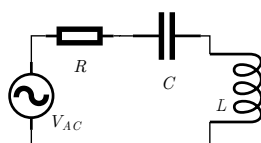

**Figure 1**

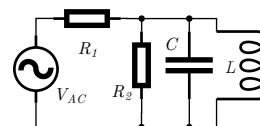

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 5 V and frequency 20 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 90 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 20 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 9 V and frequency 60 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 3 V and frequency 60 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 6 V and frequency 40 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 6 V, duty cycle 70 % and frequency 20 Hz. (0.5 point)





# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14155580</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>LUIS ALEJANDRO URBINA GONZALEZ</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.07$  s. The values are  $R = R_1 = R_2 = 60 \Omega$ ,  $L = 20$  mH,  $C = 400$   $\mu$ F and  $V_{AC} = 40$  V at 70 Hz. (3 + 3 points)

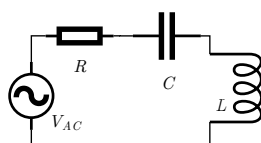

**Figure 1**

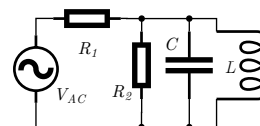

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 4 V and frequency 60 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 60 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 5 V and frequency 50 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 4 V and frequency 40 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 2 V and frequency 30 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 2 V, duty cycle 60 % and frequency 50 Hz. (0.5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón


Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	<b>14629184</b>
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<b>JOSE WALDO QUINTANA ARANDA</b>		

## Instructions


1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at  $t = 0$  s, find the instantaneous voltage and current through each element at  $t = 0.05$  s. The values are  $R = R_1 = R_2 = 50 \Omega$ ,  $L = 30$  mH,  $C = 500$   $\mu$ F and  $V_{AC} = 40$  V at 90 Hz. (3 + 3 points)

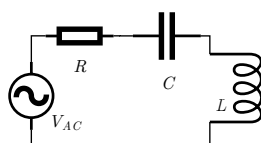

**Figure 1**

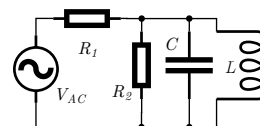

**Figure 2**

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
  - (a) Sine wave with amplitude 7 V and frequency 20 Hz. (1 point)
  - (b) Half-wave rectified sine wave with amplitude 8 V and frequency 40 Hz. (0.5 point)
  - (c) Full-wave rectified sine wave with amplitude 2 V and frequency 90 Hz. (0.5 point)
  - (d) Triangular wave with amplitude 4 V and frequency 20 Hz. (0.5 point)
  - (e) Sawtooth wave with amplitude 5 V and frequency 20 Hz. (0.5 point)
  - (f) Rectangular wave with amplitude 3 V and frequency 50 Hz. (0.5 point)
  - (g) Pulse wave with amplitude 5 V, duty cycle 20 % and frequency 30 Hz. (0.5 point)