



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14137625
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS EMMANUEL MORALES MENUIOLA		

Answers

1. (a) Figure 1

- i. $I = (0.027998 - j0.12655) \text{ A}$
- ii. $V_R = (1.3999 - j6.3275) \text{ V}$
- iii. $V_L = (33.3956 + j7.38841) \text{ V}$
- iv. $V_C = (-4.7955 - j1.0609) \text{ V}$
- v. $P_R = 0.83993 \text{ W}$
- vi. $P_L = 4.433 \text{ VAR}$
- vii. $P_C = -0.63657 \text{ VAR}$

(b) Figure 2

- i. $V_{R1} = (18.6297 + j6.42422) \text{ V}$
- ii. $V_{R2} = V_L = V_C = (11.3703 - j6.42422) \text{ V}$
- iii. $I_{R1} = (0.37259 + j0.12848) \text{ A}$
- iv. $I_{R2} = (0.22741 - j0.12848) \text{ A}$
- v. $I_L = (0.16953 + j0.30006) \text{ A}$
- vi. $I_C = (-0.024344 - j0.043087) \text{ A}$
- vii. $P_{R1} = 7.7667 \text{ W}$
- viii. $P_{R2} = 3.4111 \text{ W}$
- ix. $P_L = 0.6463 \text{ VAR}$
- x. $P_C = -4.5008 \text{ VAR}$

2. (a) $V_{R1} = (18.6297 + j6.42422) \text{ V}$

(b) $V_{R2} = V_L = V_C = (11.3703 - j6.42422) \text{ V}$

(c) $I_{R1} = (0.37259 + j0.12848) \text{ A}$

(d) $I_{R2} = (0.22741 - j0.12848) \text{ A}$

(e) $I_L = (0.16953 + j0.30006) \text{ A}$

(f) $I_C = (-0.024344 - j0.043087) \text{ A}$

(g) $P_{R1} = 7.7667 \text{ W}$

(h) $P_{R2} = 3.4111 \text{ W}$

(i) $P_L = 0.6463 \text{ VAR}$

(j) $P_C = -4.5008 \text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14121732
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOEL GERARDO AGUERO LLANAS		

Answers

1. (a) Figure 1

- i. $I = (0.493\ 64 - j0.056\ 05)\text{ A}$
- ii. $V_R = (39.4909 - j4.484\ 02)\text{ V}$
- iii. $V_L = (4.226\ 09 + j37.2193)\text{ V}$
- iv. $V_C = (-3.716\ 95 - j32.7352)\text{ V}$
- v. $P_R = 19.7454\text{ W}$
- vi. $P_L = 18.6096\text{ VAR}$
- vii. $P_C = -16.3676\text{ VAR}$

(b) Figure 2

- i. $V_{R1} = (20.1051 + j1.445\ 75)\text{ V}$
- ii. $V_{R2} = V_L = V_C = (19.8949 - j1.445\ 75)\text{ V}$
- iii. $I_{R1} = (0.251\ 31 + j0.018\ 072)\text{ A}$
- iv. $I_{R2} = (0.248\ 69 - j0.018\ 072)\text{ A}$
- v. $I_L = (0.021\ 801 + j0.300\ 01)\text{ A}$
- vi. $I_C = (-0.019\ 175 - j0.263\ 86)\text{ A}$
- vii. $P_{R1} = 5.0788\text{ W}$
- viii. $P_{R2} = 4.9737\text{ W}$
- ix. $P_L = 5.2773\text{ VAR}$
- x. $P_C = -6.0002\text{ VAR}$

2. (a) $V_{R1} = (20.1051 + j1.445\ 75)\text{ V}$

(b) $V_{R2} = V_L = V_C = (19.8949 - j1.445\ 75)\text{ V}$

(c) $I_{R1} = (0.251\ 31 + j0.018\ 072)\text{ A}$

(d) $I_{R2} = (0.248\ 69 - j0.018\ 072)\text{ A}$

(e) $I_L = (0.021\ 801 + j0.300\ 01)\text{ A}$

(f) $I_C = (-0.019\ 175 - j0.263\ 86)\text{ A}$

(g) $P_{R1} = 5.0788\text{ W}$

(h) $P_{R2} = 4.9737\text{ W}$

(i) $P_L = 5.2773\text{ VAR}$

(j) $P_C = -6.0002\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14124427
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JERSON CHAVEZ ORTIZ		

Answers

1. (a) Figure 1

- $I = (0.171\ 58 - j0.5204)\text{ A}$
- $V_R = (6.863\ 02 - j20.8161)\text{ V}$
- $V_L = (78.4749 + j25.873)\text{ V}$
- $V_C = (-15.3379 - j5.056\ 87)\text{ V}$
- $P_R = 12.0103\text{ W}$
- $P_L = 45.2777\text{ VAR}$
- $P_C = -8.8495\text{ VAR}$

(b) Figure 2

- $V_{R1} = (43.0368 + j14.7207)\text{ V}$
- $V_{R2} = V_L = V_C = (26.9632 - j14.7207)\text{ V}$
- $I_{R1} = (1.0759 + j0.368\ 02)\text{ A}$
- $I_{R2} = (0.674\ 08 - j0.368\ 02)\text{ A}$
- $I_L = (0.499\ 46 + j0.914\ 84)\text{ A}$
- $I_C = (-0.097\ 62 - j0.178\ 81)\text{ A}$
- $P_{R1} = 51.7217\text{ W}$
- $P_{R2} = 23.5928\text{ W}$
- $P_L = 6.2582\text{ VAR}$
- $P_C = -32.0194\text{ VAR}$

2. (a) $V_{R1} = (43.0368 + j14.7207)\text{ V}$

(b) $V_{R2} = V_L = V_C = (26.9632 - j14.7207)\text{ V}$

(c) $I_{R1} = (1.0759 + j0.368\ 02)\text{ A}$

(d) $I_{R2} = (0.674\ 08 - j0.368\ 02)\text{ A}$

(e) $I_L = (0.499\ 46 + j0.914\ 84)\text{ A}$

(f) $I_C = (-0.097\ 62 - j0.178\ 81)\text{ A}$

(g) $P_{R1} = 51.7217\text{ W}$

(h) $P_{R2} = 23.5928\text{ W}$

(i) $P_L = 6.2582\text{ VAR}$

(j) $P_C = -32.0194\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14156040
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ANTONIO FERNENDEZ CARRASCO		

Answers

1. (a) Figure 1

- $I = (0.083\,992 - j0.298\,22)\text{ A}$
- $V_R = (5.879\,46 - j20.8756)\text{ V}$
- $V_L = (89.9417 + j25.3315)\text{ V}$
- $V_C = (-15.8212 - j4.455\,93)\text{ V}$
- $P_R = 6.7194\text{ W}$
- $P_L = 28.9503\text{ VAR}$
- $P_C = -5.0925\text{ VAR}$

(b) Figure 2

- $V_{R1} = (49.1261 + j16.7857)\text{ V}$
- $V_{R2} = V_L = V_C = (30.8739 - j16.7857)\text{ V}$
- $I_{R1} = (0.7018 + j0.2398)\text{ A}$
- $I_{R2} = (0.441\,06 - j0.2398)\text{ A}$
- $I_L = (0.3164 + j0.581\,96)\text{ A}$
- $I_C = (-0.055\,657 - j0.102\,37)\text{ A}$
- $P_{R1} = 38.5019\text{ W}$
- $P_{R2} = 17.6422\text{ W}$
- $P_L = 4.0948\text{ VAR}$
- $P_C = -23.2784\text{ VAR}$

2. (a) $V_{R1} = (49.1261 + j16.7857)\text{ V}$

(b) $V_{R2} = V_L = V_C = (30.8739 - j16.7857)\text{ V}$

(c) $I_{R1} = (0.7018 + j0.2398)\text{ A}$

(d) $I_{R2} = (0.441\,06 - j0.2398)\text{ A}$

(e) $I_L = (0.3164 + j0.581\,96)\text{ A}$

(f) $I_C = (-0.055\,657 - j0.102\,37)\text{ A}$

(g) $P_{R1} = 38.5019\text{ W}$

(h) $P_{R2} = 17.6422\text{ W}$

(i) $P_L = 4.0948\text{ VAR}$

(j) $P_C = -23.2784\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14156037
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	MICHAEL MURILLO MENDEZ		

Answers

1. (a) Figure 1

- $I = (0.31834 + j0.069086) \text{ A}$
- $V_R = (28.6506 + j6.21775) \text{ V}$
- $V_L = (-7.81346 + j36.0034) \text{ V}$
- $V_C = (9.16283 - j42.2212) \text{ V}$
- $P_R = 9.5502 \text{ W}$
- $P_L = 12.0011 \text{ VAR}$
- $P_C = -14.0737 \text{ VAR}$

(b) Figure 2

- $V_{R1} = (15.0513 - j0.875923) \text{ V}$
- $V_{R2} = V_L = V_C = (14.9487 + j0.875923) \text{ V}$
- $I_{R1} = (0.16724 - j0.0097325) \text{ A}$
- $I_{R2} = (0.1661 + j0.0097325) \text{ A}$
- $I_L = (-0.0066043 + j0.11271) \text{ A}$
- $I_C = (0.0077449 - j0.13218) \text{ A}$
- $P_{R1} = 2.5257 \text{ W}$
- $P_{R2} = 2.4914 \text{ W}$
- $P_L = 1.9826 \text{ VAR}$
- $P_C = -1.6907 \text{ VAR}$

2. (a) $V_{R1} = (15.0513 - j0.875923) \text{ V}$

(b) $V_{R2} = V_L = V_C = (14.9487 + j0.875923) \text{ V}$

(c) $I_{R1} = (0.16724 - j0.0097325) \text{ A}$

(d) $I_{R2} = (0.1661 + j0.0097325) \text{ A}$

(e) $I_L = (-0.0066043 + j0.11271) \text{ A}$

(f) $I_C = (0.0077449 - j0.13218) \text{ A}$

(g) $P_{R1} = 2.5257 \text{ W}$

(h) $P_{R2} = 2.4914 \text{ W}$

(i) $P_L = 1.9826 \text{ VAR}$

(j) $P_C = -1.6907 \text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11073892
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSUE AMADOR SIFUENTES		

Answers

1. (a) Figure 1

- $I = (0.052\,217 - j0.244\,81)\text{ A}$
- $V_R = (2.610\,83 - j12.2406)\text{ V}$
- $V_L = (64.6046 + j13.7796)\text{ V}$
- $V_C = (-7.2154 - j1.539)\text{ V}$
- $P_R = 3.133\text{ W}$
- $P_L = 16.5356\text{ VAR}$
- $P_C = -1.8468\text{ VAR}$

(b) Figure 2

- $V_{R1} = (40.8644 + j14.4186)\text{ V}$
- $V_{R2} = V_L = V_C = (19.1356 - j14.4186)\text{ V}$
- $I_{R1} = (0.817\,29 + j0.288\,37)\text{ A}$
- $I_{R2} = (0.382\,71 - j0.288\,37)\text{ A}$
- $I_L = (0.489\,21 + j0.649\,26)\text{ A}$
- $I_C = (-0.054\,638 - j0.072\,513)\text{ A}$
- $P_{R1} = 37.5558\text{ W}$
- $P_{R2} = 11.4814\text{ W}$
- $P_L = 2.1754\text{ VAR}$
- $P_C = -19.4777\text{ VAR}$

2. (a) $V_{R1} = (40.8644 + j14.4186)\text{ V}$

(b) $V_{R2} = V_L = V_C = (19.1356 - j14.4186)\text{ V}$

(c) $I_{R1} = (0.817\,29 + j0.288\,37)\text{ A}$

(d) $I_{R2} = (0.382\,71 - j0.288\,37)\text{ A}$

(e) $I_L = (0.489\,21 + j0.649\,26)\text{ A}$

(f) $I_C = (-0.054\,638 - j0.072\,513)\text{ A}$

(g) $P_{R1} = 37.5558\text{ W}$

(h) $P_{R2} = 11.4814\text{ W}$

(i) $P_L = 2.1754\text{ VAR}$

(j) $P_C = -19.4777\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11268436
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDUARDO ZALDIVAR MARTINEZ		

Answers

1. (a) Figure 1

- i. $I = (0.11757 - j0.21204) \text{ A}$
- ii. $V_R = (9.4054 - j16.9633) \text{ V}$
- iii. $V_L = (39.9689 + j22.161) \text{ V}$
- iv. $V_C = (-9.3743 - j5.19762) \text{ V}$
- v. $P_R = 4.7027 \text{ W}$
- vi. $P_L = 11.0805 \text{ VAR}$
- vii. $P_C = -2.5988 \text{ VAR}$

(b) Figure 2

- i. $V_{R1} = (26.4833 + j9.36126) \text{ V}$
- ii. $V_{R2} = V_L = V_C = (13.5167 - j9.36126) \text{ V}$
- iii. $I_{R1} = (0.33104 + j0.11702) \text{ A}$
- iv. $I_{R2} = (0.16896 - j0.11702) \text{ A}$
- v. $I_L = (0.21175 + j0.30574) \text{ A}$
- vi. $I_C = (-0.049663 - j0.071708) \text{ A}$
- vii. $P_{R1} = 9.8625 \text{ W}$
- viii. $P_{R2} = 3.3792 \text{ W}$
- ix. $P_L = 1.4342 \text{ VAR}$
- x. $P_C = -6.1148 \text{ VAR}$

2. (a) $V_{R1} = (26.4833 + j9.36126) \text{ V}$

(b) $V_{R2} = V_L = V_C = (13.5167 - j9.36126) \text{ V}$

(c) $I_{R1} = (0.33104 + j0.11702) \text{ A}$

(d) $I_{R2} = (0.16896 - j0.11702) \text{ A}$

(e) $I_L = (0.21175 + j0.30574) \text{ A}$

(f) $I_C = (-0.049663 - j0.071708) \text{ A}$

(g) $P_{R1} = 9.8625 \text{ W}$

(h) $P_{R2} = 3.3792 \text{ W}$

(i) $P_L = 1.4342 \text{ VAR}$

(j) $P_C = -6.1148 \text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14140390
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS DAVID MARENTES REYES		

Answers

1. (a) Figure 1

- $I = (0.027\,053 - j0.113\,11)\text{ A}$
- $V_R = (1.6232 - j6.7868)\text{ V}$
- $V_L = (38.3782 + j9.178\,73)\text{ V}$
- $V_C = (-10.0013 - j2.391\,97)\text{ V}$
- $P_R = 0.811\,58\text{ W}$
- $P_L = 4.5894\text{ VAR}$
- $P_C = -1.196\text{ VAR}$

(b) Figure 2

- $V_{R1} = (15.8882 + j3.540\,27)\text{ V}$
- $V_{R2} = V_L = V_C = (14.1118 - j3.540\,27)\text{ V}$
- $I_{R1} = (0.2648 + j0.059\,005)\text{ A}$
- $I_{R2} = (0.2352 - j0.059\,005)\text{ A}$
- $I_L = (0.040\,04 + j0.1596)\text{ A}$
- $I_C = (-0.010\,434 - j0.041\,592)\text{ A}$
- $P_{R1} = 4.4161\text{ W}$
- $P_{R2} = 3.528\text{ W}$
- $P_L = 0.623\,88\text{ VAR}$
- $P_C = -2.394\text{ VAR}$

2. (a) $V_{R1} = (15.8882 + j3.540\,27)\text{ V}$

(b) $V_{R2} = V_L = V_C = (14.1118 - j3.540\,27)\text{ V}$

(c) $I_{R1} = (0.2648 + j0.059\,005)\text{ A}$

(d) $I_{R2} = (0.2352 - j0.059\,005)\text{ A}$

(e) $I_L = (0.040\,04 + j0.1596)\text{ A}$

(f) $I_C = (-0.010\,434 - j0.041\,592)\text{ A}$

(g) $P_{R1} = 4.4161\text{ W}$

(h) $P_{R2} = 3.528\text{ W}$

(i) $P_L = 0.623\,88\text{ VAR}$

(j) $P_C = -2.394\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12068799
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS ANTONIO ROBLESREYES		

Answers

1. (a) Figure 1

- $I = (0.028\,419 - j0.356\,48)\text{ A}$
- $V_R = (0.568\,39 - j7.1296)\text{ V}$
- $V_L = (120.9516 + j9.642\,469)\text{ V}$
- $V_C = (-31.5199 - j2.512\,82)\text{ V}$
- $P_R = 2.5577\text{ W}$
- $P_L = 43.3911\text{ VAR}$
- $P_C = -11.3077\text{ VAR}$

(b) Figure 2

- $V_{R1} = (45.3125 + j3.736\,96)\text{ V}$
- $V_{R2} = V_L = V_C = (44.6875 - j3.736\,96)\text{ V}$
- $I_{R1} = (2.2656 + j0.186\,85)\text{ A}$
- $I_{R2} = (2.2344 - j0.186\,85)\text{ A}$
- $I_L = (0.042\,264 + j0.5054)\text{ A}$
- $I_C = (-0.011\,014 - j0.131\,71)\text{ A}$
- $P_{R1} = 103.3594\text{ W}$
- $P_{R2} = 100.5469\text{ W}$
- $P_L = 5.9269\text{ VAR}$
- $P_C = -22.7432\text{ VAR}$

2. (a) $V_{R1} = (45.3125 + j3.736\,96)\text{ V}$

(b) $V_{R2} = V_L = V_C = (44.6875 - j3.736\,96)\text{ V}$

(c) $I_{R1} = (2.2656 + j0.186\,85)\text{ A}$

(d) $I_{R2} = (2.2344 - j0.186\,85)\text{ A}$

(e) $I_L = (0.042\,264 + j0.5054)\text{ A}$

(f) $I_C = (-0.011\,014 - j0.131\,71)\text{ A}$

(g) $P_{R1} = 103.3594\text{ W}$

(h) $P_{R2} = 100.5469\text{ W}$

(i) $P_L = 5.9269\text{ VAR}$

(j) $P_C = -22.7432\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14150725
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LILIANA VERA GLZ		

Answers

1. (a) Figure 1

- $I = (0.076\ 828 - j0.3107)\text{ A}$
- $V_R = (2.3048 - j9.321)\text{ V}$
- $V_L = (46.8525 + j11.5854)\text{ V}$
- $V_C = (-9.1573 - j2.2644)\text{ V}$
- $P_R = 3.0731\text{ W}$
- $P_L = 15.4471\text{ VAR}$
- $P_C = -3.0191\text{ VAR}$

(b) Figure 2

- $V_{R1} = (22.8718 + j7.013\ 43)\text{ V}$
- $V_{R2} = V_L = V_C = (17.1282 - j7.013\ 43)\text{ V}$
- $I_{R1} = (0.762\ 39 + j0.233\ 78)\text{ A}$
- $I_{R2} = (0.570\ 94 - j0.233\ 78)\text{ A}$
- $I_L = (0.237\ 96 + j0.581\ 15)\text{ A}$
- $I_C = (-0.046\ 509 - j0.113\ 59)\text{ A}$
- $P_{R1} = 19.0769\text{ W}$
- $P_{R2} = 11.4188\text{ W}$
- $P_L = 2.2717\text{ VAR}$
- $P_C = -11.6229\text{ VAR}$

2. (a) $V_{R1} = (22.8718 + j7.013\ 43)\text{ V}$

(b) $V_{R2} = V_L = V_C = (17.1282 - j7.013\ 43)\text{ V}$

(c) $I_{R1} = (0.762\ 39 + j0.233\ 78)\text{ A}$

(d) $I_{R2} = (0.570\ 94 - j0.233\ 78)\text{ A}$

(e) $I_L = (0.237\ 96 + j0.581\ 15)\text{ A}$

(f) $I_C = (-0.046\ 509 - j0.113\ 59)\text{ A}$

(g) $P_{R1} = 19.0769\text{ W}$

(h) $P_{R2} = 11.4188\text{ W}$

(i) $P_L = 2.2717\text{ VAR}$

(j) $P_C = -11.6229\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14125016
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	DAVID OTHONIEL SALDIVAR PEREZ		

Answers

1. (a) Figure 1

- $I = (0.2073 - j0.16164) \text{ A}$
- $V_R = (12.4382 - j9.69821) \text{ V}$
- $V_L = (18.2807 + j23.4454) \text{ V}$
- $V_C = (-10.7189 - j13.7472) \text{ V}$
- $P_R = 4.1461 \text{ W}$
- $P_L = 7.8151 \text{ VAR}$
- $P_C = -4.5824 \text{ VAR}$

(b) Figure 2

- $V_{R1} = (10.3383 + j1.808) \text{ V}$
- $V_{R2} = V_L = V_C = (9.6617 - j1.808) \text{ V}$
- $I_{R1} = (0.17231 + j0.030133) \text{ A}$
- $I_{R2} = (0.16103 - j0.030133) \text{ A}$
- $I_L = (0.027264 + j0.14569) \text{ A}$
- $I_C = (-0.015986 - j0.085428) \text{ A}$
- $P_{R1} = 1.8358 \text{ W}$
- $P_{R2} = 1.6103 \text{ W}$
- $P_L = 0.85428 \text{ VAR}$
- $P_C = -1.4569 \text{ VAR}$

2. (a) $V_{R1} = (10.3383 + j1.808) \text{ V}$

(b) $V_{R2} = V_L = V_C = (9.6617 - j1.808) \text{ V}$

(c) $I_{R1} = (0.17231 + j0.030133) \text{ A}$

(d) $I_{R2} = (0.16103 - j0.030133) \text{ A}$

(e) $I_L = (0.027264 + j0.14569) \text{ A}$

(f) $I_C = (-0.015986 - j0.085428) \text{ A}$

(g) $P_{R1} = 1.8358 \text{ W}$

(h) $P_{R2} = 1.6103 \text{ W}$

(i) $P_L = 0.85428 \text{ VAR}$

(j) $P_C = -1.4569 \text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	1205596
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ALBERTO VAZQUEZ MEDINA		

Answers

1. (a) Figure 1

- $I = (0.25069 - j0.3538) \text{ A}$
- $V_R = (20.0554 - j28.3038) \text{ V}$
- $V_L = (53.3514 + j37.8036) \text{ V}$
- $V_C = (-13.4068 - j9.49975) \text{ V}$
- $P_R = 15.0416 \text{ W}$
- $P_L = 28.3527 \text{ VAR}$
- $P_C = -7.1248 \text{ VAR}$

(b) Figure 2

- $V_{R1} = (41.5339 + j14.5941) \text{ V}$
- $V_{R2} = V_L = V_C = (18.4661 - j14.5941) \text{ V}$
- $I_{R1} = (0.51917 + j0.18243) \text{ A}$
- $I_{R2} = (0.23083 - j0.18243) \text{ A}$
- $I_L = (0.38513 + j0.48731) \text{ A}$
- $I_C = (-0.09678 - j0.12246) \text{ A}$
- $P_{R1} = 24.2257 \text{ W}$
- $P_{R2} = 6.9248 \text{ W}$
- $P_L = 3.6737 \text{ VAR}$
- $P_C = -14.6192 \text{ VAR}$

2. (a) $V_{R1} = (41.5339 + j14.5941) \text{ V}$

(b) $V_{R2} = V_L = V_C = (18.4661 - j14.5941) \text{ V}$

(c) $I_{R1} = (0.51917 + j0.18243) \text{ A}$

(d) $I_{R2} = (0.23083 - j0.18243) \text{ A}$

(e) $I_L = (0.38513 + j0.48731) \text{ A}$

(f) $I_C = (-0.09678 - j0.12246) \text{ A}$

(g) $P_{R1} = 24.2257 \text{ W}$

(h) $P_{R2} = 6.9248 \text{ W}$

(i) $P_L = 3.6737 \text{ VAR}$

(j) $P_C = -14.6192 \text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12666518
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	SAMUEL ROSAS GONZALEZ		

Answers

1. (a) Figure 1

- $I = (1.3113 - j2.0448) \text{ A}$
- $V_R = (26.2252 - j40.8963) \text{ V}$
- $V_L = (154.1755 + j98.8668) \text{ V}$
- $V_C = (-90.40069 - j57.9705) \text{ V}$
- $P_R = 118.0136 \text{ W}$
- $P_L = 444.9006 \text{ VAR}$
- $P_C = -260.8672 \text{ VAR}$

(b) Figure 2

- $V_{R1} = (45.3905 + j4.17391) \text{ V}$
- $V_{R2} = V_L = V_C = (44.6095 - j4.17391) \text{ V}$
- $I_{R1} = (2.2695 + j0.2087) \text{ A}$
- $I_{R2} = (2.2305 - j0.2087) \text{ A}$
- $I_L = (0.094412 + j1.009) \text{ A}$
- $I_C = (-0.055358 - j0.59165) \text{ A}$
- $P_{R1} = 103.8861 \text{ W}$
- $P_{R2} = 100.3713 \text{ W}$
- $P_L = 26.6243 \text{ VAR}$
- $P_C = -45.4069 \text{ VAR}$

2. (a) $V_{R1} = (45.3905 + j4.17391) \text{ V}$

(b) $V_{R2} = V_L = V_C = (44.6095 - j4.17391) \text{ V}$

(c) $I_{R1} = (2.2695 + j0.2087) \text{ A}$

(d) $I_{R2} = (2.2305 - j0.2087) \text{ A}$

(e) $I_L = (0.094412 + j1.009) \text{ A}$

(f) $I_C = (-0.055358 - j0.59165) \text{ A}$

(g) $P_{R1} = 103.8861 \text{ W}$

(h) $P_{R2} = 100.3713 \text{ W}$

(i) $P_L = 26.6243 \text{ VAR}$

(j) $P_C = -45.4069 \text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12064655
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDSON ORLANDONAVARRO RAMIREZ		

Answers

1. (a) Figure 1

- $I = (0.18755 - j0.28643) \text{ A}$
- $V_R = (15.0036 - j22.9145) \text{ V}$
- $V_L = (53.9909 + j35.3514) \text{ V}$
- $V_C = (-18.9945 - j12.437) \text{ V}$
- $P_R = 9.3773 \text{ W}$
- $P_L = 22.0946 \text{ VAR}$
- $P_C = -7.7731 \text{ VAR}$

(b) Figure 2

- $V_{R1} = (28.3149 + j8.47843) \text{ V}$
- $V_{R2} = V_L = V_C = (21.6851 - j8.47843) \text{ V}$
- $I_{R1} = (0.35394 + j0.10598) \text{ A}$
- $I_{R2} = (0.27106 - j0.10598) \text{ A}$
- $I_L = (0.12785 + j0.327) \text{ A}$
- $I_C = (-0.044979 - j0.11504) \text{ A}$
- $P_{R1} = 10.9202 \text{ W}$
- $P_{R2} = 6.7766 \text{ W}$
- $P_L = 2.8761 \text{ VAR}$
- $P_C = -8.1751 \text{ VAR}$

2. (a) $V_{R1} = (28.3149 + j8.47843) \text{ V}$

(b) $V_{R2} = V_L = V_C = (21.6851 - j8.47843) \text{ V}$

(c) $I_{R1} = (0.35394 + j0.10598) \text{ A}$

(d) $I_{R2} = (0.27106 - j0.10598) \text{ A}$

(e) $I_L = (0.12785 + j0.327) \text{ A}$

(f) $I_C = (-0.044979 - j0.11504) \text{ A}$

(g) $P_{R1} = 10.9202 \text{ W}$

(h) $P_{R2} = 6.7766 \text{ W}$

(i) $P_L = 2.8761 \text{ VAR}$

(j) $P_C = -8.1751 \text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11126870
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN GAEL GONZALEZ RODRIGUEZ		

Answers

1. (a) Figure 1

- $I = (0.008\,299\,8 - j0.128\,57)\text{ A}$
- $V_R = (0.166 - j2.5714)\text{ V}$
- $V_L = (43.6234 + j2.816\,06)\text{ V}$
- $V_C = (-3.7894 - j0.244\,62)\text{ V}$
- $P_R = 0.331\,99\text{ W}$
- $P_L = 5.6321\text{ VAR}$
- $P_C = -0.489\,24\text{ VAR}$

(b) Figure 2

- $V_{R1} = (21.7516 + j5.653\,69)\text{ V}$
- $V_{R2} = V_L = V_C = (18.2484 - j5.653\,69)\text{ V}$
- $I_{R1} = (1.0876 + j0.282\,68)\text{ A}$
- $I_{R2} = (0.912\,42 - j0.282\,68)\text{ A}$
- $I_L = (0.191\,83 + j0.619\,15)\text{ A}$
- $I_C = (-0.016\,663 - j0.053\,784)\text{ A}$
- $P_{R1} = 25.2549\text{ W}$
- $P_{R2} = 18.2484\text{ W}$
- $P_L = 1.0757\text{ VAR}$
- $P_C = -12.3831\text{ VAR}$

2. (a) $V_{R1} = (21.7516 + j5.653\,69)\text{ V}$

(b) $V_{R2} = V_L = V_C = (18.2484 - j5.653\,69)\text{ V}$

(c) $I_{R1} = (1.0876 + j0.282\,68)\text{ A}$

(d) $I_{R2} = (0.912\,42 - j0.282\,68)\text{ A}$

(e) $I_L = (0.191\,83 + j0.619\,15)\text{ A}$

(f) $I_C = (-0.016\,663 - j0.053\,784)\text{ A}$

(g) $P_{R1} = 25.2549\text{ W}$

(h) $P_{R2} = 18.2484\text{ W}$

(i) $P_L = 1.0757\text{ VAR}$

(j) $P_C = -12.3831\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14155580
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ALEJANDRO URBINA GONZALEZ		

Answers

1. (a) Figure 1

- $I = (0.033\,086 - j0.162\,72)\text{ A}$
- $V_R = (1.9851 - j9.763)\text{ V}$
- $V_L = (55.2085 + j11.2257)\text{ V}$
- $V_C = (-7.1937 - j1.4627)\text{ V}$
- $P_R = 1.6543\text{ W}$
- $P_L = 9.3548\text{ VAR}$
- $P_C = -1.2189\text{ VAR}$

(b) Figure 2

- $V_{R1} = (31.4581 + j10.9428)\text{ V}$
- $V_{R2} = V_L = V_C = (18.5419 - j10.9428)\text{ V}$
- $I_{R1} = (0.5243 + j0.182\,38)\text{ A}$
- $I_{R2} = (0.309\,03 - j0.182\,38)\text{ A}$
- $I_L = (0.247\,52 + j0.419\,41)\text{ A}$
- $I_C = (-0.032\,252 - j0.054\,649)\text{ A}$
- $P_{R1} = 18.4892\text{ W}$
- $P_{R2} = 7.7258\text{ W}$
- $P_L = 1.3662\text{ VAR}$
- $P_C = -10.4852\text{ VAR}$

2. (a) $V_{R1} = (31.4581 + j10.9428)\text{ V}$

(b) $V_{R2} = V_L = V_C = (18.5419 - j10.9428)\text{ V}$

(c) $I_{R1} = (0.5243 + j0.182\,38)\text{ A}$

(d) $I_{R2} = (0.309\,03 - j0.182\,38)\text{ A}$

(e) $I_L = (0.247\,52 + j0.419\,41)\text{ A}$

(f) $I_C = (-0.032\,252 - j0.054\,649)\text{ A}$

(g) $P_{R1} = 18.4892\text{ W}$

(h) $P_{R2} = 7.7258\text{ W}$

(i) $P_L = 1.3662\text{ VAR}$

(j) $P_C = -10.4852\text{ VAR}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14629184
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSE WALDO QUINTANA ARANDA		

Answers

1. (a) Figure 1

- $I = (0.0071741 - j0.084396) \text{ A}$
- $V_R = (0.14348 - j1.6879) \text{ V}$
- $V_L = (25.4532 + j2.16367) \text{ V}$
- $V_C = (-5.5967 - j0.47575) \text{ V}$
- $P_R = 0.14348 \text{ W}$
- $P_L = 2.1637 \text{ VAR}$
- $P_C = -0.47575 \text{ VAR}$

(b) Figure 2

- $V_{R1} = (10.1365 + j1.16033) \text{ V}$
- $V_{R2} = V_L = V_C = (9.8635 - j1.1603) \text{ V}$
- $I_{R1} = (0.50683 + j0.058017) \text{ A}$
- $I_{R2} = (0.49317 - j0.058017) \text{ A}$
- $I_L = (0.017497 + j0.14874) \text{ A}$
- $I_C = (-0.0038474 - j0.032705) \text{ A}$
- $P_{R1} = 5.2048 \text{ W}$
- $P_{R2} = 4.9317 \text{ W}$
- $P_L = 0.32705 \text{ VAR}$
- $P_C = -1.4874 \text{ VAR}$

2. (a) $V_{R1} = (10.1365 + j1.16033) \text{ V}$

(b) $V_{R2} = V_L = V_C = (9.8635 - j1.1603) \text{ V}$

(c) $I_{R1} = (0.50683 + j0.058017) \text{ A}$

(d) $I_{R2} = (0.49317 - j0.058017) \text{ A}$

(e) $I_L = (0.017497 + j0.14874) \text{ A}$

(f) $I_C = (-0.0038474 - j0.032705) \text{ A}$

(g) $P_{R1} = 5.2048 \text{ W}$

(h) $P_{R2} = 4.9317 \text{ W}$

(i) $P_L = 0.32705 \text{ VAR}$

(j) $P_C = -1.4874 \text{ VAR}$