



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón

|                  |                                      |                |                 |
|------------------|--------------------------------------|----------------|-----------------|
| Subject          | Industrial electronics               | Group          | 9B              |
| Degree           | Mechanical engineering               | Date           | 09/02/2017      |
| Exam / Homework  | Homework 2: Transistors              | Registration # | <b>12717949</b> |
| Professor's name | Suresh Kumar Gadi                    | Marks Obtained | ____ / 10       |
| Student's name   | <b>JUAN CARLOS BARRIENTOS GUERRA</b> |                |                 |

## Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Design a circuit with transistor to realize an amplifier. (5 point)
2. Design a circuit with transistor to realize an switch. (5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón

|                  |   |                |                |
|------------------|---|----------------|----------------|
| Subject          | Industrial electronics                    | Group          | 9B             |
| Degree           | Mechanical engineering                    | Date           | 09/02/2017     |
| Exam / Homework  | Homework 2: Transistors                   | Registration # | <b>8062187</b> |
| Professor's name | Suresh Kumar Gadi                         | Marks Obtained | ____ / 10      |
| Student's name   | <b>PÉREZ-FIGUEROA MAEDA CARLOS ARTURO</b> |                |                |

## Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Design a circuit with transistor to realize an amplifier. (5 point)
2. Design a circuit with transistor to realize an switch. (5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón

|                  |                               |                |                 |
|------------------|-------------------------------|----------------|-----------------|
| Subject          | Industrial electronics        | Group          | 9B              |
| Degree           | Mechanical engineering        | Date           | 09/02/2017      |
| Exam / Homework  | Homework 2: Transistors       | Registration # | <b>12112592</b> |
| Professor's name | Suresh Kumar Gadi             | Marks Obtained | ____ / 10       |
| Student's name   | <b>ROGELIO FLORES SALAZAR</b> |                |                 |

## Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Design a circuit with transistor to realize an amplifier. (5 point)
2. Design a circuit with transistor to realize an switch. (5 point)



# Universidad Autónoma de Coahuila

## Facultad de Ingeniería Mecánica y Eléctrica

### Unidad Torreón

|                  |  |                |                 |
|------------------|--|----------------|-----------------|
| Subject          | Industrial electronics                 | Group          | 9B              |
| Degree           | Mechanical engineering                 | Date           | 09/02/2017      |
| Exam / Homework  | Homework 2: Transistors                | Registration # | <b>12122623</b> |
| Professor's name | Suresh Kumar Gadi                      | Marks Obtained | ____ / 10       |
| Student's name   | <b>RAÚL ALEXANDRO ARELLANO SALCIDO</b> |                |                 |

## Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on a A4 or a letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

## Questions

1. Design a circuit with transistor to realize an amplifier. (5 point)
2. Design a circuit with transistor to realize an switch. (5 point)