



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14137625
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS EMMANUEL MORALES MENUOLA		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 5$ s. The values are $R = R_1 = R_2 = 40 \Omega$, $L = 0.05$ H, $C = 20 \mu\text{F}$ and $V_{AC} = 50$ V at 90 Hz. (3 + 3 points)

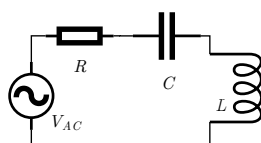


Figure 1

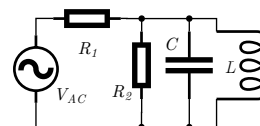


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 7 V and frequency 50 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 7 V and frequency 70 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 3 V and frequency 40 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 3 V and frequency 50 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 2 V and frequency 90 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 9 V and frequency 50 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 4 V, duty cycle 50 % and frequency 80 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14121732
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOEL GERARDO AGUERO LLANAS		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 2$ s. The values are $R = R_1 = R_2 = 50 \Omega$, $L = 0.09$ H, $C = 60 \mu\text{F}$ and $V_{AC} = 70$ V at 20 Hz. (3 + 3 points)

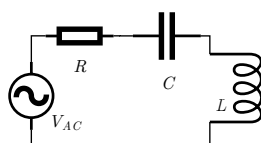


Figure 1

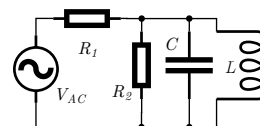


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 9 V and frequency 80 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 2 V and frequency 40 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 70 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 5 V and frequency 60 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 8 V and frequency 50 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 5 V and frequency 70 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 6 V, duty cycle 20 % and frequency 70 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14124427
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JERSON CHAVEZ ORTIZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 5$ s. The values are $R = R_1 = R_2 = 60 \Omega$, $L = 0.03$ H, $C = 90 \mu\text{F}$ and $V_{AC} = 70$ V at 30 Hz. (3 + 3 points)

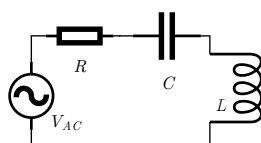


Figure 1

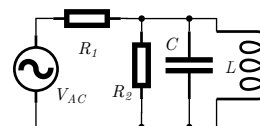


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 6 V and frequency 40 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 4 V and frequency 90 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 7 V and frequency 20 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 8 V and frequency 80 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 8 V and frequency 80 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 5 V and frequency 70 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 3 V, duty cycle 40 % and frequency 80 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14156040
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ANTONIO FERNENDEZ CARRASCO		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 7$ s. The values are $R = R_1 = R_2 = 80 \Omega$, $L = 0.05$ H, $C = 40 \mu\text{F}$ and $V_{AC} = 60$ V at 90 Hz. (3 + 3 points)

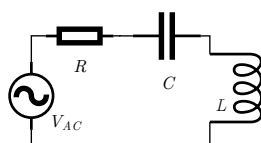


Figure 1

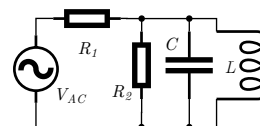


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 3 V and frequency 70 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 8 V and frequency 50 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 8 V and frequency 60 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 2 V and frequency 50 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 4 V and frequency 30 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 6 V, duty cycle 70 % and frequency 20 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14156037
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	MICHAEL MURILLO MENDEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 6$ s. The values are $R = R_1 = R_2 = 90 \Omega$, $L = 0.06$ H, $C = 70 \mu\text{F}$ and $V_{AC} = 20$ V at 70 Hz. (3 + 3 points)

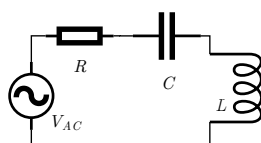


Figure 1

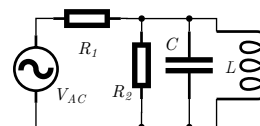


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 8 V and frequency 90 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 3 V and frequency 20 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 3 V and frequency 90 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 5 V and frequency 30 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 4 V and frequency 90 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 2 V and frequency 40 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 6 V, duty cycle 90 % and frequency 50 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11073892
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSUE AMADOR SIFUENTES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 2$ s. The values are $R = R_1 = R_2 = 90 \Omega$, $L = 0.06$ H, $C = 50 \mu\text{F}$ and $V_{AC} = 40$ V at 90 Hz. (3 + 3 points)

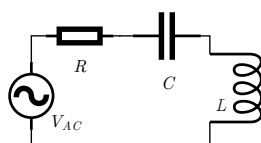


Figure 1

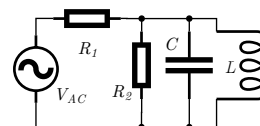


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 5 V and frequency 50 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 7 V and frequency 90 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 6 V and frequency 30 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 7 V and frequency 80 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 5 V and frequency 60 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 9 V and frequency 40 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 8 V, duty cycle 40 % and frequency 70 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11268436
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDUARDO ZALDIVAR MARTINEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 4$ s. The values are $R = R_1 = R_2 = 70 \Omega$, $L = 0.02$ H, $C = 50 \mu\text{F}$ and $V_{AC} = 50$ V at 40 Hz. (3 + 3 points)

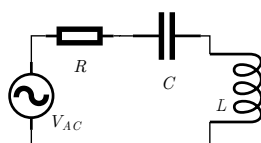


Figure 1

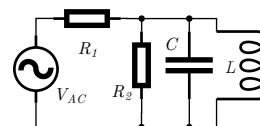


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 8 V and frequency 80 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 5 V and frequency 60 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 30 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 8 V and frequency 20 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 7 V and frequency 90 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 2 V and frequency 70 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 7 V, duty cycle 90 % and frequency 20 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14140390
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS DAVID MARENTES REYES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 3$ s. The values are $R = R_1 = R_2 = 80 \Omega$, $L = 0.07$ H, $C = 30 \mu\text{F}$ and $V_{AC} = 70$ V at 80 Hz. (3 + 3 points)

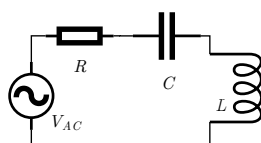


Figure 1

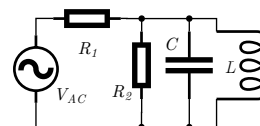


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 3 V and frequency 60 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 30 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 3 V and frequency 80 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 4 V and frequency 30 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 2 V and frequency 90 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 8 V and frequency 70 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 2 V, duty cycle 80 % and frequency 30 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12068799
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS ANTONIO ROBLESREYES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 5$ s. The values are $R = R_1 = R_2 = 50 \Omega$, $L = 0.02$ H, $C = 30 \mu\text{F}$ and $V_{AC} = 70$ V at 40 Hz. (3 + 3 points)

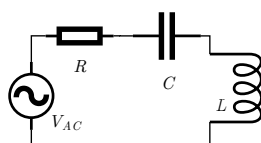


Figure 1

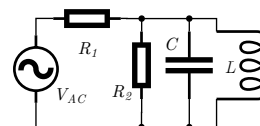


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 6 V and frequency 20 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 30 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 9 V and frequency 20 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 6 V and frequency 70 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 7 V and frequency 40 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 2 V and frequency 70 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 8 V, duty cycle 60 % and frequency 30 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14150725
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LILIANA VERA GLZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 5$ s. The values are $R = R_1 = R_2 = 30 \Omega$, $L = 0.04$ H, $C = 60 \mu\text{F}$ and $V_{AC} = 90$ V at 40 Hz. (3 + 3 points)

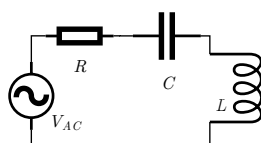


Figure 1

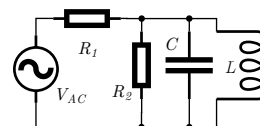


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 5 V and frequency 30 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 4 V and frequency 90 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 60 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 9 V and frequency 30 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 9 V and frequency 90 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 4 V and frequency 70 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 7 V, duty cycle 60 % and frequency 20 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14125016
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	DAVID OTHONIEL SALDIVAR PEREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 2$ s. The values are $R = R_1 = R_2 = 30 \Omega$, $L = 0.06$ H, $C = 90 \mu\text{F}$ and $V_{AC} = 50$ V at 40 Hz. (3 + 3 points)

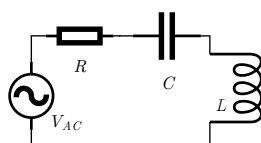


Figure 1

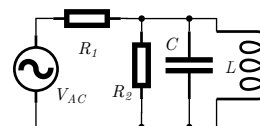


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 5 V and frequency 60 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 3 V and frequency 40 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 2 V and frequency 70 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 7 V and frequency 40 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 2 V and frequency 20 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 7 V and frequency 60 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 6 V, duty cycle 30 % and frequency 70 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	1205596
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ALBERTO VAZQUEZ MEDINA		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 8$ s. The values are $R = R_1 = R_2 = 50 \Omega$, $L = 0.07$ H, $C = 70 \mu\text{F}$ and $V_{AC} = 80$ V at 60 Hz. (3 + 3 points)

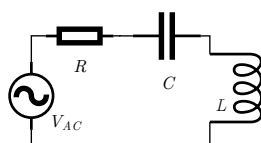


Figure 1

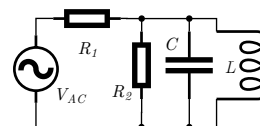


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 8 V and frequency 80 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 4 V and frequency 70 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 6 V and frequency 70 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 7 V and frequency 90 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 7 V and frequency 40 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 6 V, duty cycle 20 % and frequency 60 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12666518
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	SAMUEL ROSAS GONZALEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 3$ s. The values are $R = R_1 = R_2 = 50 \Omega$, $L = 0.07$ H, $C = 90 \mu\text{F}$ and $V_{AC} = 50$ V at 70 Hz. (3 + 3 points)

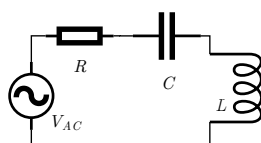


Figure 1

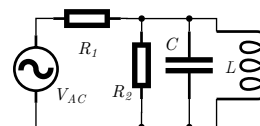


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 4 V and frequency 20 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 2 V and frequency 60 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 9 V and frequency 70 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 8 V and frequency 40 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 6 V and frequency 80 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 4 V, duty cycle 70 % and frequency 70 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12064655
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDSON ORLANDONAVARRO RAMIREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 7$ s. The values are $R = R_1 = R_2 = 70 \Omega$, $L = 0.09$ H, $C = 60 \mu\text{F}$ and $V_{AC} = 90$ V at 40 Hz. (3 + 3 points)

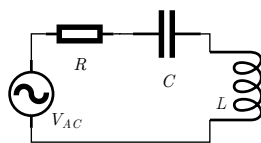


Figure 1

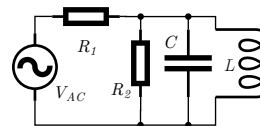


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 4 V and frequency 80 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 5 V and frequency 40 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 5 V and frequency 40 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 3 V and frequency 30 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 7 V and frequency 80 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 3 V and frequency 70 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 9 V, duty cycle 30 % and frequency 50 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11126870
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN GAEL GONZALEZ RODRIGUEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 6$ s. The values are $R = R_1 = R_2 = 60 \Omega$, $L = 0.08$ H, $C = 80 \mu\text{F}$ and $V_{AC} = 90$ V at 90 Hz. (3 + 3 points)

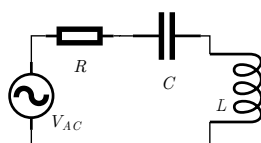


Figure 1

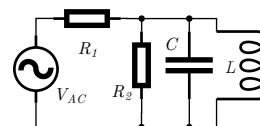


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 5 V and frequency 20 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 90 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 4 V and frequency 20 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 9 V and frequency 60 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 3 V and frequency 60 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 6 V and frequency 40 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 6 V, duty cycle 70 % and frequency 20 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14155580
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ALEJANDRO URBINA GONZALEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 7$ s. The values are $R = R_1 = R_2 = 60 \Omega$, $L = 0.02$ H, $C = 40 \mu\text{F}$ and $V_{AC} = 40$ V at 70 Hz. (3 + 3 points)

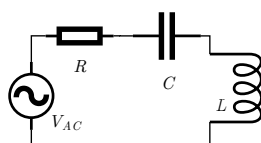


Figure 1

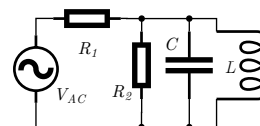


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 4 V and frequency 60 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 9 V and frequency 60 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 5 V and frequency 50 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 4 V and frequency 80 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 4 V and frequency 40 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 2 V and frequency 30 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 2 V, duty cycle 60 % and frequency 50 Hz. (0.5 point)



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14629184
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSE WALDO QUINTANA ARANDA		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Draw the phase diagram, waveforms for the voltage across each element and current through each element of the circuits shown in Figure 1 and Figure 2. Ignoring the transient behavior and considering that the reference is the input voltage, which starts its zero at $t = 0$ s, find the instantaneous voltage and current through each element at $t = 5$ s. The values are $R = R_1 = R_2 = 50 \Omega$, $L = 0.03$ H, $C = 50 \mu\text{F}$ and $V_{AC} = 40$ V at 90 Hz. (3 + 3 points)

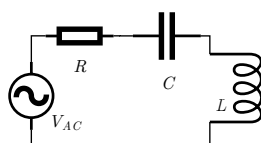


Figure 1

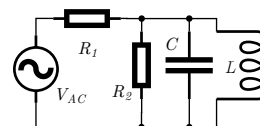


Figure 2

2. Find root mean square (RMS), average rectified value (ARV), peak factor, form factor for the following periodic functions. Show all the work. (4 points)
 - (a) Sine wave with amplitude 7 V and frequency 20 Hz. (1 point)
 - (b) Half-wave rectified sine wave with amplitude 8 V and frequency 40 Hz. (0.5 point)
 - (c) Full-wave rectified sine wave with amplitude 2 V and frequency 90 Hz. (0.5 point)
 - (d) Triangular wave with amplitude 4 V and frequency 20 Hz. (0.5 point)
 - (e) Sawtooth wave with amplitude 5 V and frequency 20 Hz. (0.5 point)
 - (f) Rectangular wave with amplitude 3 V and frequency 50 Hz. (0.5 point)
 - (g) Pulse wave with amplitude 5 V, duty cycle 20 % and frequency 30 Hz. (0.5 point)