



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14137625
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS EMMANUEL MORALES MENUIOLA		

Answers

1. $R_{AB} = (1.2148 + j2.5503) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14121732
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOEL GERARDO AGUERO LLANAS		

Answers

1. $R_{AB} = (2.9217 + j3.7458) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14124427
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JERSON CHAVEZ ORTIZ		

Answers

1. $R_{AB} = (4.0508 + j2.7107) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14156040
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<i>LUIS ANTNONIO FERNENDEZ CARRASCO</i>		

Answers

1. $R_{AB} = (2.4229 + j3.04) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14156037
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	MICHAEL MURILLO MENDEZ		

Answers

1. $R_{AB} = (3.7712 + j1.3111) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	11073892
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSUE AMADOR SIFUENTES		

Answers

1. $R_{AB} = (2.817 + j2.1883) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	11268436
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDUARDO ZALDIVAR MARTINEZ		

Answers

1. $R_{AB} = (2.8733 + j2.2459) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14140390
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS DAVID MARENTES REYES		

Answers

1. $R_{AB} = (1.9577 + j3.6735) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	12068799
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS ANTONIO ROBLESREYES		

Answers

1. $R_{AB} = (2.2353 + j2.9412) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14150725
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LILIANA VERA GLZ		

Answers

1. $R_{AB} = (2.4054 + j3.4324) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14125016
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	DAVID OTHONIEL SALDIVAR PEREZ		

Answers

1. $R_{AB} = (3.5944 + j3.0739) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	1205596
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ALBERTO VAZQUEZ MEDINA		

Answers

1. $R_{AB} = (3.1985 + j3.8747) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	12666518
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	SAMUEL ROSAS GONZALEZ		

Answers

1. $R_{AB} = (4.0383 + j2.9585) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	12064655
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDSON ORLANDONAVARRO RAMIREZ		

Answers

1. $R_{AB} = (3.12 + j4.5067) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	11126870
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN GAEL GONZALEZ RODRIGUEZ		

Answers

1. $R_{AB} = (3.7054 + j4.3739) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14155580
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ALEJANDRO URBINA GONZALEZ		

Answers

1. $R_{AB} = (2.3014 + j1.863) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica
Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	4/10/2016
Exam / Homework	Homework 3: Nodal and Mesh analysis	Registration #	14629184
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSE WALDO QUINTANA ARANDA		

Answers

1. $R_{AB} = (2.5132 + j1.8664) \Omega$
2. There are no electric currents in the circuit.
3. There are no electric currents in the circuit.