



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14137625
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS EMMANUEL MORALES MENUIOLA		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14121732
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOEL GERARDO AGUERO LLANAS		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14124427
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JERSON CHAVEZ ORTIZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14156040
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<i>LUIS ANTONIO FERNENDEZ CARRASCO</i>		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14156037
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	MICHAEL MURILLO MENDEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11073892
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSUE AMADOR SIFUENTES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11268436
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDUARDO ZALDIVAR MARTINEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14140390
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS DAVID MARENTES REYES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12068799
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS ANTONIO ROBLESREYES		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14150725
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LILIANA VERA GLZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14125016
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	DAVID OTHONIEL SALDIVAR PEREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	1205596
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ALBERTO VAZQUEZ MEDINA		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12666518
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	SAMUEL ROSAS GONZALEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	12064655
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDSON ORLANDONAVARRO RAMIREZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	11126870
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN GAEL GONZALEZ RODRIGUEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	15/09/2016
Exam / Homework	Homework 2: A.C. Fundamentals	Registration #	14155580
Professor's name	Dr. Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ALEJANDRO URBINA GONZALEZ		

Instructions

1. The student should submit the homework on or before the due date. (LATE SUBMISSION = 0 MARKS)
2. Answers should be hand written on the A4 or Letter size bond papers. (20% of the marks obtained will be reduced)
3. The student should print his/her corresponding question-paper and staple it along with his/her answer sheets. (20% of the marks obtained will be reduced)
4. In the calculations, the student should maintain at least a precision of 3 decimal places with a correct rounding. (20% of the marks obtained will be reduced)

Questions

1. Plot phase diagram, voltage and current waveforms for the