



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14137625
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS EMMANUEL MORALES MENUIOLA		

Answers

- $297 + 908j$
 - $63.0328 + 22.3607j$
 - $6.8276 + 6.069j$
 - $1.0265 + 0.50387j$
- 67.5Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.10085 - 0.23888j) \text{ A}$
 - $V_R = (9.07683 - 21.4993j) \text{ V}$
 - $V_L = (72.0449 + 30.4167j) \text{ V}$
 - $V_C = (-21.1217 - 8.91742j) \text{ V}$
 - $P_R = (-4.2204 - 4.3366j) \text{ W}$
 - $P_L = (14.532 - 14.1425j) \text{ W}$
 - $P_C = (-4.2604 + 4.1462j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14121732
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOEL GERARDO AGUERO LLANAS		

Answers

- $-142 - 65j$
 - $-26 + 51j$
 - $2.4779 + 5.1681j$
 - $0.16837 + 0.51818j$
- 7.5Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.096035 - 0.38838j) \text{ A}$
 - $V_R = (2.88104 - 11.6513j) \text{ V}$
 - $V_L = (58.5656 + 14.4817j) \text{ V}$
 - $V_C = (-11.4466 - 2.83045j) \text{ V}$
 - $P_R = (-4.2484 - 2.2379j) \text{ W}$
 - $P_L = (11.2487 - 21.3547j) \text{ W}$
 - $P_C = (-2.1985 + 4.1738j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14124427
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JERSON CHAVEZ ORTIZ		

Answers

1. (a) $-1001 + 664j$
(b) $-3.494\,118 + 116.2235j$
(c) $3.0333 + 8.5667j$
(d) $0.765\,24 + 0.895\,55j$
2. $12.5\,\Omega$
3. $R(1 + \sqrt{3})$
4. (a) Figure 3
 - i. $I = (0.398\,79 - 0.610\,48j)\,\text{A}$
 - ii. $V_R = (11.9637 - 18.3144j)\,\text{V}$
 - iii. $V_L = (46.0291 + 30.0679j)\,\text{V}$
 - iv. $V_C = (-17.9928 - 11.7535j)\,\text{V}$
 - v. $P_R = (-6.4096 - 14.6071j)\,\text{W}$
 - vi. $P_L = (36.7118 - 16.1091j)\,\text{W}$
 - vii. $P_C = (-14.3506 + 6.297\,04j)\,\text{W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14156040
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	<i>LUIS ANTONIO FERNENDEZ CARRASCO</i>		

Answers

- $-835 + 88j$
 - $-33.2787 + 64.9344j$
 - $6.4634 + 6.1707j$
 - $0.5686 + 0.90601j$
- 10Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.082454 - 0.27505j) \text{ A}$
 - $V_R = (2.4736 - 8.2516j) \text{ V}$
 - $V_L = (51.8465 + 15.5421j) \text{ V}$
 - $V_C = (-24.3202 - 7.2905j) \text{ V}$
 - $P_R = (-2.0657 - 1.3608j) \text{ W}$
 - $P_L = (8.54987 - 12.9791j) \text{ W}$
 - $P_C = (-4.0106 + 6.0882j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14156037
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	MICHAEL MURILLO MENDEZ		

Answers

- $-432 + 432j$
 - $63.6923 + 66.4615j$
 - $4.7765 + 6.4941j$
 - $0.59986 + 0.73188j$
- 8.3333Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.07466 - 0.33746j) \text{ A}$
 - $V_R = (3.73302 - 16.8732j) \text{ V}$
 - $V_L = (89.0549 + 19.7024j) \text{ V}$
 - $V_C = (-12.7879 - 2.82919j) \text{ V}$
 - $P_R = (-5.4154 - 2.5195j) \text{ W}$
 - $P_L = (13.2978 - 28.5819j) \text{ W}$
 - $P_C = (-1.9095 + 4.1042j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	11073892
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JOSUE AMADOR SIFUENTES		

Answers

- $-72 + 368j$
 - $56.4 + 27.2j$
 - $3.3103 + 4.2759j$
 - $0.62868 + 0.50595j$
- 26.6667Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.10098 - 0.20073j) \text{ A}$
 - $V_R = (8.07873 - 16.0587j) \text{ V}$
 - $V_L = (37.8375 + 19.0351j) \text{ V}$
 - $V_C = (-5.9163 - 2.9763j) \text{ V}$
 - $P_R = (-2.4077 - 3.2434j) \text{ W}$
 - $P_L = (7.642 - 5.6731j) \text{ W}$
 - $P_C = (-1.1949 + 0.88704j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	11268436
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDUARDO ZALDIVAR MARTINEZ		

Answers

1. (a) $-936 + 352j$
(b) $-37.169\,23 + 110.9538j$
(c) $7.9888 + 4.382j$
(d) $0.658\,74 + 0.869\,17j$
2. $35\,\Omega$
3. $R(1 + \sqrt{3})$
4. (a) Figure 3
 - i. $I = (0.174\,54 - 0.1393j)\,\text{A}$
 - ii. $V_R = (12.2178 - 9.750\,96j)\,\text{V}$
 - iii. $V_L = (26.2573 + 32.9001j)\,\text{V}$
 - iv. $V_C = (-18.4752 - 23.1492j)\,\text{V}$
 - v. $P_R = (0.774\,21 - 3.4039j)\,\text{W}$
 - vi. $P_L = (9.1659 + 2.0848j)\,\text{W}$
 - vii. $P_C = (-6.4493 - 1.4669j)\,\text{W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14140390
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS DAVID MARENTES REYES		

Answers

1. (a) $154 + 414j$
(b) $36.2162 + 15.2973j$
(c) $6.2941 + 6.8235j$
(d) $0.80022 + 0.37305j$
2. 11.6667Ω
3. $R(1 + \sqrt{3})$
4. (a) Figure 3
 - i. $I = (0.10152 - 0.21841j) \text{ A}$
 - ii. $V_R = (7.10639 - 15.289j) \text{ V}$
 - iii. $V_L = (41.1702 + 19.136j) \text{ V}$
 - iv. $V_C = (-8.2766 - 3.847j) \text{ V}$
 - v. $P_R = (-2.6179 - 3.1043j) \text{ W}$
 - vi. $P_L = (8.35919 - 7.0495j) \text{ W}$
 - vii. $P_C = (-1.6805 + 1.4172j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12068799
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JESUS ANTONIO ROBLESREYES		

Answers

- $-936 + 352j$
 - $-23.3425 + 70.2466j$
 - $4.5 + 7.5j$
 - $0.68938 + 0.9132j$
- 12.5Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.27458 - 0.6883j) \text{ A}$
 - $V_R = (8.23731 - 20.6491j) \text{ V}$
 - $V_L = (77.8453 + 31.0539j) \text{ V}$
 - $V_C = (-26.0826 - 10.4048j) \text{ V}$
 - $P_R = (-11.9511 - 11.3395j) \text{ W}$
 - $P_L = (42.7491 - 45.0545j) \text{ W}$
 - $P_C = (-14.3234 + 15.0958j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14150725
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LILIANA VERA GLZ		

Answers

1. (a) $-198 + 10j$
(b) $-9.0566 + 49.6981j$
(c) $2.5385 + 7.0256j$
(d) $0.29242 + 0.54513j$
2. 15Ω
3. $R(1 + \sqrt{3})$
4. (a) Figure 3
 - i. $I = (1.6437 - 1.4931j) \text{ A}$
 - ii. $V_R = (32.8744 - 29.862j) \text{ V}$
 - iii. $V_L = (225.154 + 247.867j) \text{ V}$
 - iv. $V_C = (-198.0284 - 218.005j) \text{ V}$
 - v. $P_R = (9.44934 - 98.1694j) \text{ W}$
 - vi. $P_L = (740.1799 + 71.24637j) \text{ W}$
 - vii. $P_C = (-651.0061 - 62.6629j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14125016
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	DAVID OTHONIEL SALDIVAR PEREZ		

Answers

1. (a) $-414 - 154j$
(b) $-45.76 + 41.32j$
(c) $8.646\,02 + 6.309\,73j$
(d) $0.337\,92 + 0.769\,64j$
2. $33.3333\,\Omega$
3. $R(1 + \sqrt{3})$
4. (a) Figure 3
 - i. $I = (0.321\,65 - 0.158\,75j)\,\text{A}$
 - ii. $V_R = (16.0823 - 7.937\,58j)\,\text{V}$
 - iii. $V_L = (17.9544 + 36.3774j)\,\text{V}$
 - iv. $V_C = (-14.0367 - 28.4398j)\,\text{V}$
 - v. $P_R = (3.9127 - 5.1062j)\,\text{W}$
 - vi. $P_L = (11.5499 + 8.850\,39j)\,\text{W}$
 - vii. $P_C = (-9.029\,73 - 6.919\,23j)\,\text{W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	1205596
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	ALBERTO VAZQUEZ MEDINA		

Answers

- $-908 - 297j$
 - $-29.566 + 30.0189j$
 - $7.2 + 9.1j$
 - $0.47666 + 1.066j$
- 20.8333Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.036112 - 0.1427j) \text{ A}$
 - $V_R = (1.8056 - 7.135j) \text{ V}$
 - $V_L = (37.6574 + 9.52971j) \text{ V}$
 - $V_C = (-9.463 - 2.3947j) \text{ V}$
 - $P_R = (-0.95295 - 0.51531j) \text{ W}$
 - $P_L = (2.7198 - 5.0296j) \text{ W}$
 - $P_C = (-0.68346 + 1.2639j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12666518
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	SAMUEL ROSAS GONZALEZ		

Answers

- $-236 + 115j$
 - $-15.7 + 51.1j$
 - $2.7059 + 5.6765j$
 - $0.43584 + 0.53295j$
- 46.6667Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.18978 - 0.35588j) \text{ A}$
 - $V_R = (13.2849 - 24.9119j) \text{ V}$
 - $V_L = (93.91582 + 50.08284j) \text{ V}$
 - $V_C = (-47.2007 - 25.1709j) \text{ V}$
 - $P_R = (-6.34453 - 9.45578j) \text{ W}$
 - $P_L = (35.6475 - 23.9183j) \text{ W}$
 - $P_C = (-17.9159 + 12.021j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	12064655
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	EDSON ORLANDONAVARRO RAMIREZ		

Answers

- $-250 + 250j$
 - $30 + 60j$
 - $4.641 + 7.1282j$
 - $0.50588 + 0.57647j$
- 5Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (1.7839 - 2.2012j) \text{ A}$
 - $V_R = (35.6789 - 44.0241j) \text{ V}$
 - $V_L = (248.9501 + 201.7594j) \text{ V}$
 - $V_C = (-194.629 - 157.7353j) \text{ V}$
 - $P_R = (-33.25667 - 157.0729j) \text{ W}$
 - $P_L = (888.2266 - 188.0621j) \text{ W}$
 - $P_C = (-694.4149 + 147.0268j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	11126870
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	JUAN GAEL GONZALEZ RODRIGUEZ		

Answers

1. (a) $-835 + 88j$
(b) $-33.2787 + 64.9344j$
(c) $6.4634 + 6.1707j$
(d) $0.5686 + 0.90601j$
2. 10Ω
3. $R(1 + \sqrt{3})$
4. (a) Figure 3
 - i. $I = (0.082454 - 0.27505j) \text{ A}$
 - ii. $V_R = (2.4736 - 8.2516j) \text{ V}$
 - iii. $V_L = (51.8465 + 15.5421j) \text{ V}$
 - iv. $V_C = (-24.3202 - 7.2905j) \text{ V}$
 - v. $P_R = (-2.0657 - 1.3608j) \text{ W}$
 - vi. $P_L = (8.54987 - 12.9791j) \text{ W}$
 - vii. $P_C = (-4.0106 + 6.0882j) \text{ W}$



Universidad Autónoma de Coahuila

Facultad de Ingeniería Mecánica y Eléctrica

Unidad Torreón

Subject	Circuit analysis II	Group	5A
Degree	Electrical engineering	Due for	01/09/2016
Exam / Homework	Homework 1: Basics of DC and AC circuits	Registration #	14155580
Professor's name	Suresh Kumar Gadi	Marks Obtained	____ / 10
Student's name	LUIS ALEJANDRO URBINA GONZALEZ		

Answers

- $-1001 + 664j$
 - $-39.18 + 88.24j$
 - $7.16438 + 7.56164j$
 - $0.81773 + 0.88478j$
- 13.3333Ω
- $R(1 + \sqrt{3})$
- Figure 3
 - $I = (0.042678 - 0.28902j) \text{ A}$
 - $V_R = (0.85356 - 5.7805j) \text{ V}$
 - $V_L = (54.4796 + 8.0446j) \text{ V}$
 - $V_C = (-15.3332 - 2.26413j) \text{ V}$
 - $P_R = (-1.6343 - 0.4934j) \text{ W}$
 - $P_L = (4.65015 - 15.4025j) \text{ W}$
 - $P_C = (-1.3088 + 4.335j) \text{ W}$